


TWO PORT NETWORK

Port \Rightarrow A pair of terminal is known as port.

Single port Network \rightarrow If a n/w consist of one pair of terminal or two terminal is known as single port n/w.



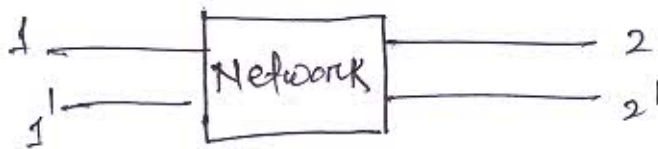
Two port Network \rightarrow The n/w having two pairs of terminal or four terminals is known as two port n/w.



\rightarrow In case of two port network, if one pair act as input port (1-1') and the other pair act as output port (2-2')

n-port Network \rightarrow If a network having n-pairs of terminals or 2n terminals is known as n-port n/w.

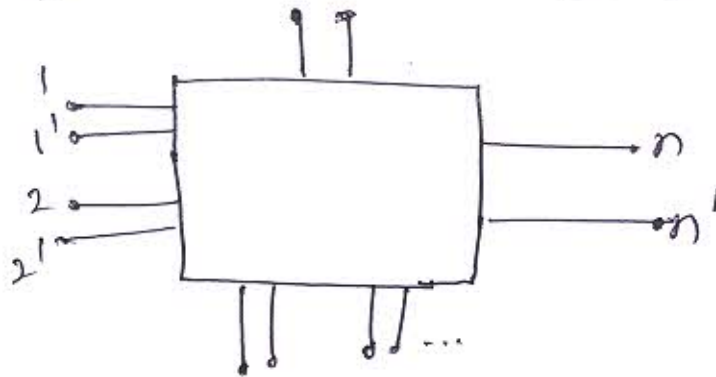\rightarrow In n-port n/w, some of them act as input port and some of them act as output port.




Parameter Representation of Two-port Network →

The relationship between V_1, I_1, V_2, I_2 can be represented in different parameter form i.e. Z-parameter, Y-parameter, h-parameter, ABCD (Transmission) parameters.

Representation of Z-parameter (open-ckt parameter)

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

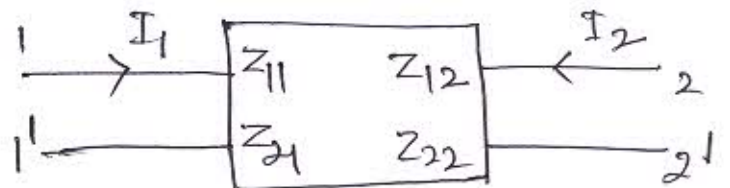

The parameters can be obtained as

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}, \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}, \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$


→ The Z-parameters are also known as open circuit parameters because all the parameters are obtained by opening input port ($I_2=0$) or opening the output port ($I_1=0$).

Representation of Y-parameters.

(short-circuit parameters) \rightarrow

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

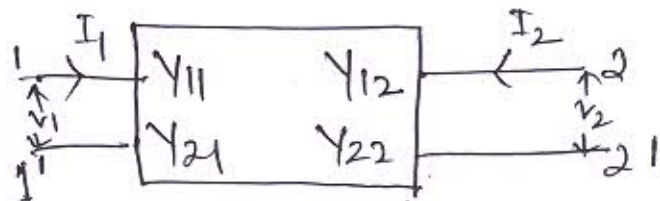

The parameters can be obtained as.

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}, \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}, \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$


\rightarrow The above parameters are also known

as short-circuit parameters because we are obtaining all the parameters by short-circuiting the input port ($V_2=0$) or by short-circuiting the output port ($V_1=0$).

Representation of h-parameters / Hybrid parameters \rightarrow

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

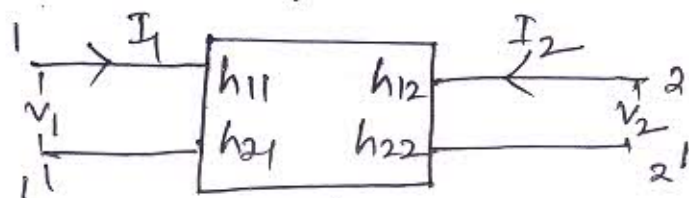

The parameters can be obtained as.

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}, \quad h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$


$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}, \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

The h-parameters are obtained by the combination of Z-parameters and Y-parameters and constant for which, they are called as hybrid parameters.

Representation of ABCD parameters. →

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

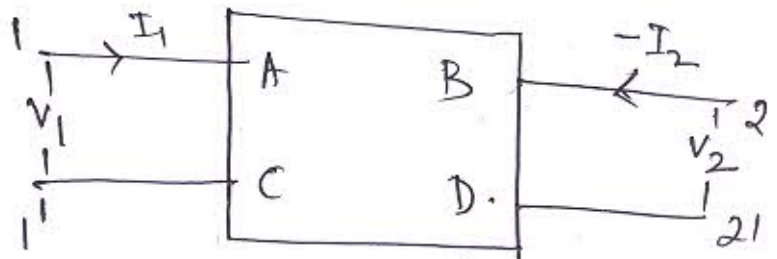

The parameters can be obtained as.


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}, \quad B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}, \quad D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

The above parameters calculated are used in Transmission lines for which they are known as Transmission parameters.

Solved Example.

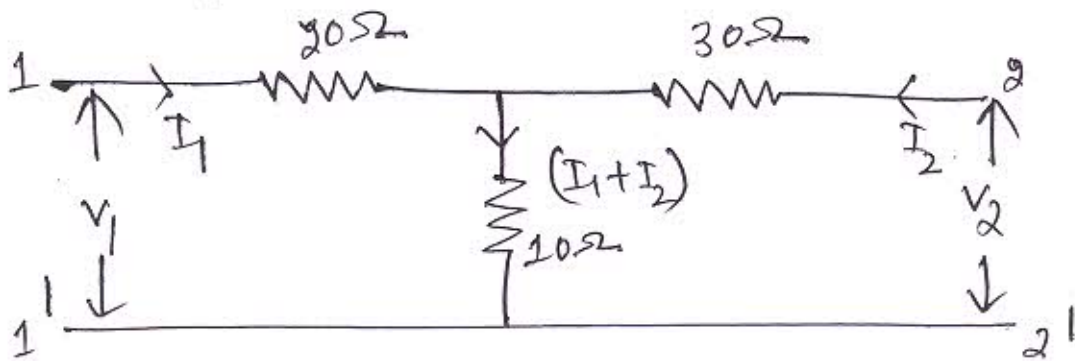(1) Determine the Z-parameters for the network shown in figure?



Solution As per the formula.

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{11} = \frac{20 \cdot I_1 + 10 \cdot I_1}{I_1} = \frac{30I_1}{I_1}$$

$$\Rightarrow \boxed{Z_{11} = 30\Omega}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$= \frac{10I_1}{I_1} = 10\Omega$$

$$\boxed{Z_{21} = 10\Omega}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$\Rightarrow Z_{22} = \frac{10I_2 + 30I_2}{I_2}$$

$$\Rightarrow Z_{22} = \frac{40I_2}{I_2} = 40\Omega$$

$$\boxed{Z_{22} = 40\Omega}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$= \frac{10I_2}{I_2} = 10\Omega$$

$$\boxed{Z_{12} = 10\Omega}$$

INTER-RELATIONSHIPS BETWEEN PARAMETERS OF TWO PORT-NETWORK

Case-I. Z parameters in Terms of Y-parameters

Z being the impedance and Y being the admittance.

$$[Z] = [Y]^{-1}$$

$$\Rightarrow \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1}$$

$$\boxed{\begin{aligned} Z_{11} &= \frac{Y_{22}}{\Delta Y} & , & \quad Z_{12} = -\frac{Y_{12}}{\Delta Y} \\ Z_{21} &= -\frac{Y_{21}}{\Delta Y} & \text{and} & \quad Z_{22} = \frac{Y_{11}}{\Delta Y} \end{aligned}}$$

$$\text{Here } \Delta Y = \begin{vmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{vmatrix} = Y_{11}Y_{22} - Y_{12}Y_{21}$$

Case-II Z parameter in Terms of ABCD parameter.

ABCD parameter equations are.

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (2)}$$

From equation (2) we get.

$$V_2 = \left(\frac{1}{C}\right)I_1 + \left(\frac{D}{C}\right)I_2 \quad \text{--- (3)}$$

From equation (1) we get.

$$V_1 = A \left[\left(\frac{1}{C}\right)I_1 + \left(\frac{D}{C}\right)I_2 \right] - BI_2$$

$$\Rightarrow V_1 = \left(\frac{A}{C}\right)I_1 + \left(\frac{AD - BC}{C}\right)I_2 \quad \text{--- (4)}$$

Comparing equⁿ (4) and (3) with Z-parameter equation.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

and $V_2 = Z_{21} I_1 + Z_{22} I_2$, we get.

$$\boxed{\begin{aligned} Z_{11} &= \frac{A}{c}, & Z_{12} &= \frac{AD - BC}{c} = \frac{AT}{c} \\ Z_{21} &= \frac{1}{c}, & Z_{22} &= \frac{D}{c}. \end{aligned}}$$

Case - III Z-parameter in terms of Hybrid parameters.

h-parameter equations are

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

From second equation.

$$V_2 = \left(-\frac{h_{21}}{h_{22}} \right) I_1 + \left(\frac{1}{h_{22}} \right) I_2 \quad \text{--- (3)}$$

From first equation.

$$V_1 = h_{11} I_1 + h_{12} \left[\left(-\frac{h_{21}}{h_{22}} \right) I_1 + \left(\frac{1}{h_{22}} \right) I_2 \right]$$

$$\Rightarrow V_1 = \left(\frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right) I_1 + \left(\frac{h_{12}}{h_{22}} \right) I_2 \quad \text{--- (4)}$$

Comparing eqnⁿ (4) and (3) with z-parameter equation.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

and $V_2 = Z_{21} I_1 + Z_{22} I_2$, we get.

$$Z_{11} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} = \frac{\Delta h}{h_{22}}$$

$$Z_{12} = \frac{h_{12}}{h_{22}}, \quad Z_{21} = -\frac{h_{21}}{h_{22}}, \quad Z_{22} = \frac{1}{h_{22}}$$

Problem calculate the z-parameters, if the values of other parameters are given below.

(a) Given $A = 2, B = -1, C = 3$ and $D = -2$.

Solution: $Z_{11} = \frac{A}{C} = \frac{2}{3} \Omega$

$$Z_{12} = \frac{\Delta T}{C} = \frac{AD - BC}{C} = \frac{-4 + 3}{3} = -\frac{1}{3} \Omega$$

$$Z_{21} = \frac{1}{C} = \frac{1}{3} \Omega$$

$$Z_{22} = \frac{D}{C} = -\frac{2}{3} \Omega$$

(b) given $h_{11} = 1$, $h_{12} = -2$, $h_{21} = -3$, $h_{22} = 2$.

Soluⁿ $Z_{11} = \frac{\Delta h}{h_{22}} = \frac{h_{11}h_{22} - h_{21}h_{12}}{h_{22}} = \frac{2 - 6}{2} = -2 \Omega$

$$Z_{12} = \frac{h_{12}}{h_{22}} = -1 \Omega$$

$$Z_{21} = \frac{-h_{21}}{h_{22}} = \frac{3}{2} \Omega$$

$$Z_{22} = \frac{1}{h_{22}} = \frac{1}{2} \Omega$$

(c) given $Y_{11} = \frac{1}{3}$, $Y_{12} = \frac{2}{3}$, $Y_{21} = -\frac{1}{3}$, $Y_{22} = \frac{1}{6}$

Soluⁿ $Z_{11} = \frac{Y_{22}}{\Delta Y} = \frac{1}{6} \times \frac{18}{5} = \frac{3}{5} \Omega$

Because $\Delta Y = Y_{11}Y_{22} - Y_{12}Y_{21} = \frac{1}{18} + \frac{2}{9} = \frac{5}{18}$

$$Z_{12} = \frac{-Y_{12}}{\Delta Y} = -\frac{2}{3} \times \frac{18}{5} = -\frac{12}{5} \Omega$$

$$Z_{21} = \frac{-Y_{21}}{\Delta Y} = \frac{1}{3} \times \frac{18}{5} = \frac{6}{5} \Omega$$

$$Z_{22} = \frac{Y_{11}}{\Delta Y} = \frac{1}{3} \times \frac{18}{5} = \frac{6}{5} \Omega$$

CONDITION FOR SYMMETRY \rightarrow

\rightarrow A two port network is said to be symmetrical if the ports can be interchanged without changing port voltages or currents.

(a) in terms of z-parameters.

$$\boxed{Z_{11} = Z_{22}}$$

(b) in terms of y-parameters.

$$\boxed{Y_{11} = Y_{22}}$$

(c) in terms of h' parameters.

$$\boxed{\Delta h = 1} \quad \text{or} \quad \begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} = 1.$$

(d) in terms of ABCD parameters.

$$\boxed{A = D.}$$

CONDITION FOR RECIPROCAL \rightarrow

\rightarrow A network is said to be reciprocal if the ratio of the response to the excitation remains same to an interchange of the positions of the excitations and response in the network.

(a) in terms of z-parameters.

$$\boxed{Z_{12} = Z_{21}}$$

(b) in terms of Y-parameters.

$$Y_{12} = Y_{21}$$

(c) in terms of h' parameters.


$$h_{12} = -h_{21}$$

(d) in terms of ABCD parameters.

$$\Delta T = 1 \quad \text{or} \quad AD - BC = 1$$

$$\text{or} \quad \begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1$$

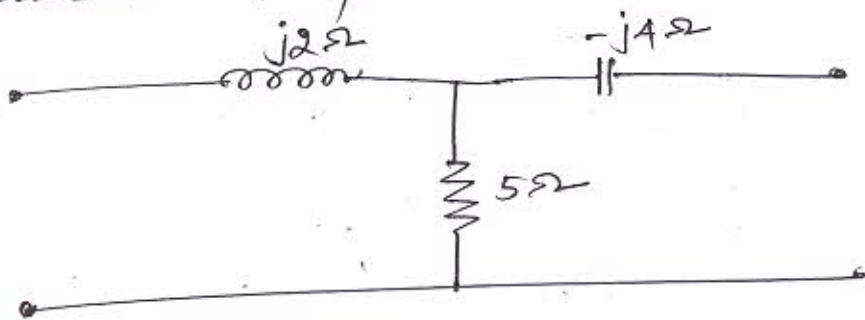
Example Forc the network shown in figure
Calculate T-parameters.



Soluⁿ T-parameters equations are.

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$
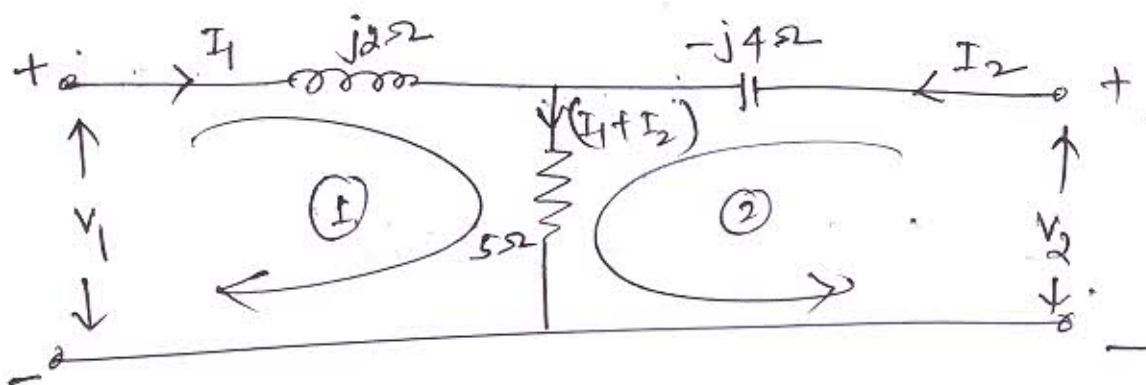
$$I_1 = CV_2 - DI_2 \quad \text{--- (2)}$$



By KVL in Loop (1) $-j2 \times I_1 - 5(I_1 + I_2) + V_1 = 0$

$$\Rightarrow V_1 = (5 + j2)I_1 + 5I_2 \quad \text{--- (3)}$$

By KVL in Loop (2) $+j4I_2 - 5(I_1 + I_2) + V_2 = 0$.

$$\Rightarrow V_2 = 5I_1 + (5 - j4)I_2 \quad \text{--- (4)}$$

Putting I_1 from equation (4) in equation (3)
we get.

$$V_1 = (5 + j2) \left[\frac{V_2 - I_2(5 - j4)}{5} \right] + 5I_2$$

$$\Rightarrow V_1 = \left(\frac{5 + j2}{5} \right) V_2 - \left[\frac{(5 + j2)(5 - j4)}{5} - 5 \right] I_2 \quad \text{--- (5)}$$

For making as equation (2), rearrange equation (A) we get.

$$I_1 = \frac{1}{5} V_2 - \left(\frac{5-j4}{5} \right) I_2 \quad \text{--- (6)}$$

To obtain T-parameters.
Comparing equⁿ (1) and (5) we get.

$$A = \left(\frac{5+j2}{5} \right), \quad B = \frac{(5+j2)(5-j4)}{5} - 5$$

$$= \left(\frac{8-j10}{5} \right)$$

Comparing equations (2) and (6) we get:

$$C = \left(\frac{1}{5} \right), \quad D = \left(\frac{5-j4}{5} \right)$$

