


TWO PORT NETWORK

Port → A pair of terminal is known as port.

Single port Network → If a n/w consist of one pair of terminal or two terminal is known as single port n/w.



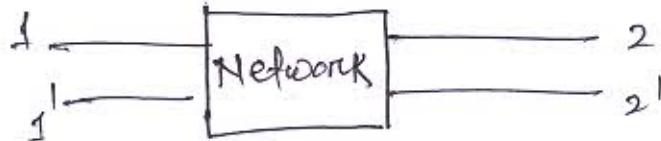
Two port Network → The n/w having two pairs of terminal or four terminals is known as two port n/w.



→ In case of two port network, if one pair act as input port ( $1-1'$ ) and the other pair act as output port ( $2-2'$ )

n-port Network → If a network having n-pairs of terminals or  $2n$  terminals is known as n-port n/w.

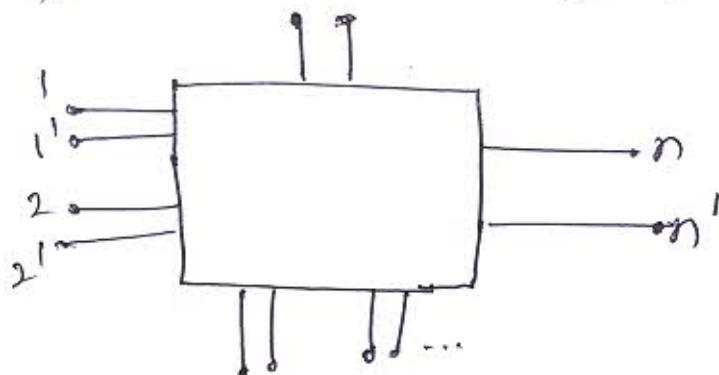→ In n-port n/w, some of them act as input port and some of them act as output port.



## Parameters Representation of Two-port Network


The relationship between  $V_1, I_1, V_2, I_2$  can be represented in different parameters form i.e.  
 $Z$ -parameters,  $\gamma$ -parameters.

$h$ -parameters, ABCD (Transmission) parameters.

### Representation of Z-parameter (open-ckt parameters)

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

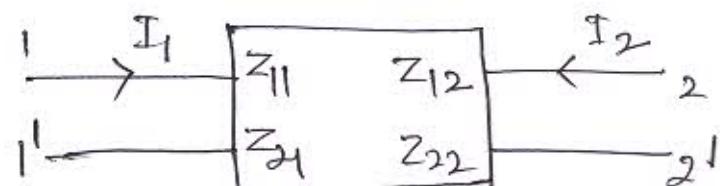

The parameters can be obtained as

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}, \quad Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$


→ The  $Z$ -parameters are also known as open circuit parameters because all the parameters are obtained by opening input port ( $I_1=0$ ) or opening the output port ( $I_2=0$ ).

Representation of Y-parameter.

(short-circuit parameters) :→

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

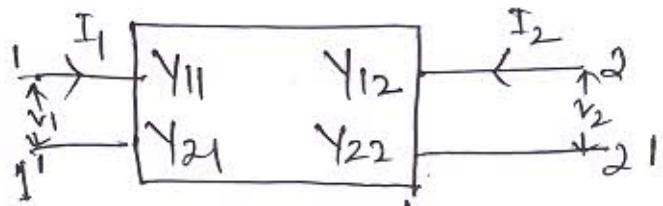

The parameters can be obtained as.

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}, \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$


$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}, \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

→ The above parameters are also known as short-circuit parameters because we are obtaining all the parameters by short-circuiting the input port ( $V_1=0$ ) or by short circuiting the output port ( $V_2=0$ ).

Representation of h-parameter / Hybrid parameter:

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

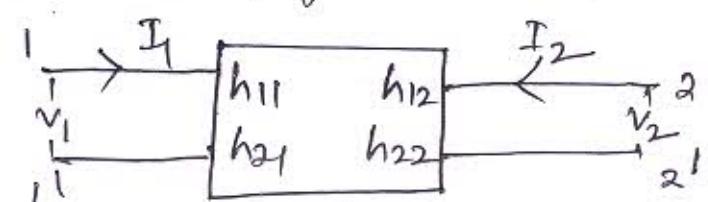

The parameters can be obtained as.

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}, \quad h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$


$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}, \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

The h-parameters are obtained by the combination of z-parameter and y-parameter and constant for which, they are called as hybrid parameters.

Representation of ABCD parameters. →

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

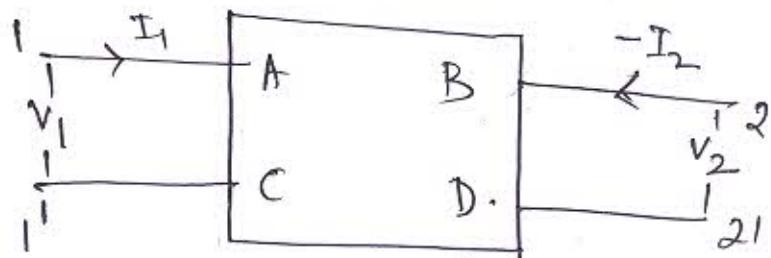

The parameters can be obtained as.


$$A = \frac{V_1}{V_2} \Big|_{I_2=0}, \quad B = \frac{V_1}{-I_2} \Big|_{V_2=0}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}, \quad D = \frac{I_1}{-I_2} \Big|_{V_2=0}$$

The above parameters calculated are used in Transmission lines for which they are known as Transmission parameters.

Solved Example.

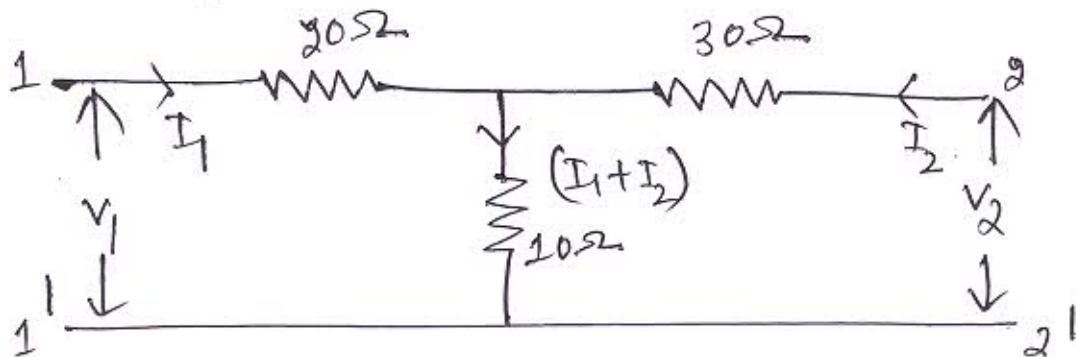(1) Determine the Z-parameter for the network shown in figure?



Solution As per the formula.

$$Z_{11} = \frac{V_1}{I_1} \mid I_2 = 0$$

$$Z_{11} = \frac{20 \cdot I_1 + 10 \cdot I_1}{I_1} = \frac{30I_1}{I_1}$$

$$\Rightarrow \boxed{Z_{11} = 30 \Omega}$$

$$Z_{21} = \frac{V_2}{I_1} \mid I_2 = 0$$

$$= \frac{10I_1}{I_1} = 10 \Omega$$

$$\boxed{Z_{21} = 10 \Omega}$$

$$Z_{22} = \frac{V_2}{I_2} \mid I_1 = 0$$

$$\Rightarrow Z_{22} = \frac{10I_2 + 30I_2}{I_2}$$

$$\Rightarrow Z_{22} = \frac{40I_2}{I_2} = 40 \Omega$$

$$\boxed{Z_{22} = 40 \Omega}$$

$$Z_{12} = \frac{V_1}{I_2} \mid I_1 = 0$$

$$= \frac{10I_2}{I_2} = 10 \Omega$$

$$\boxed{Z_{12} = 10 \Omega}$$

# INTER-RELATIONSHIPS BETWEEN PARAMETERS OF TWO PORT-NETWORK

Case-I: Z parameters in terms of Y-parameters

Z being the impedance and Y being the admittance.

$$[Z] = [Y]^{-1}$$

$$\Rightarrow \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1}$$

$$z_{11} = \frac{y_{22}}{\Delta Y}, \quad z_{12} = -\frac{y_{12}}{\Delta Y}$$

$$z_{21} = -\frac{y_{21}}{\Delta Y} \quad \text{and} \quad z_{22} = \frac{y_{11}}{\Delta Y}$$

Hence  $\Delta Y = \begin{vmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{vmatrix} = y_{11}y_{22} - y_{12}y_{21}$

Case-II: Z parameters in terms of ABCD parameters.

ABCD parameter equations are:

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (2)}$$

From equation (2) we get:

$$V_2 = \left(\frac{1}{C}\right)I_1 + \left(\frac{D}{C}\right)I_2 \quad \text{--- (3)}$$

From equation (1) we get:

$$V_1 = A \left[ \left(\frac{1}{C}\right)I_1 + \left(\frac{D}{C}\right)I_2 \right] - BI_2$$

$$\Rightarrow V_1 = \left(\frac{A}{C}\right)I_1 + \left(\frac{AD - BC}{C}\right)I_2 \quad \text{--- (4)}$$

Comparing equ<sup>n</sup> (4) and (3) with Z-parameter equation.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

and  $V_2 = Z_{21} I_1 + Z_{22} I_2$ , we get.

$$Z_{11} = \frac{A}{c}, \quad Z_{12} = \frac{AD - BC}{c} = \frac{AT}{c}$$

$$Z_{21} = \frac{1}{c}, \quad Z_{22} = \frac{D}{c}$$

### Case - III Z-parameter in terms of Hybrid parameters.

h-parameter equations are

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad (2)$$

From second equation.

$$V_2 = \left( -\frac{h_{21}}{h_{22}} \right) I_1 + \left( \frac{1}{h_{22}} \right) I_2 \quad (3)$$

From first equation.

$$V_1 = h_{11} I_1 + h_{12} \left[ \left( -\frac{h_{21}}{h_{22}} \right) I_1 + \left( \frac{1}{h_{22}} \right) I_2 \right]$$

$$\Rightarrow V_1 = \left( \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right) I_1 + \left( \frac{h_{12}}{h_{22}} \right) I_2 \quad (4)$$

Comparing eqn (4) and (3) with  
Z-parameter equation.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

and  $V_2 = Z_{21} I_1 + Z_{22} I_2$ , we get

$$Z_{11} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} = \frac{\Delta h}{h_{22}}$$

$$Z_{12} = \frac{h_{12}}{h_{22}}, Z_{21} = -\frac{h_{21}}{h_{22}}, Z_{22} = \frac{1}{h_{22}}$$

Problem calculate the z-parameters, if the values  
of other parameters are given below.

(a) Given  $A = 2$ ,  $B = -1$ ,  $C = 3$  and  $D = -2$ .

Solution:  $Z_{11} = \frac{A}{C} = \frac{2}{3} \Omega$

$$Z_{12} = \frac{\Delta T}{C} = \frac{AD - BC}{C} = -\frac{4+3}{3} = -\frac{1}{3} \Omega$$

$$Z_{21} = \frac{1}{C} = \frac{1}{3} \Omega$$

$$Z_{22} = \frac{D}{C} = -\frac{2}{3} \Omega$$

(b) Given  $h_{11} = 1, h_{12} = -2, h_{21} = -3, h_{22} = 2$ .

$$\underline{\text{Soln}} \quad Z_{11} = \frac{\Delta h}{h_{22}} = \frac{h_{11}h_{22} - h_{21}h_{12}}{h_{22}} = \frac{2-6}{2} = -2$$

$$Z_{12} = \frac{h_{12}}{h_{22}} = -1$$

$$Z_{21} = \frac{-h_{21}}{h_{22}} = \frac{3}{2}$$

$$Z_{22} = \frac{1}{h_{22}} = \frac{1}{2}$$

(c) Given  $Y_{11} = \frac{1}{3}, Y_{12} = \frac{2}{3}, Y_{21} = -\frac{1}{3}, Y_{22} = \frac{1}{6}$

$$\underline{\text{Soln}} \quad Z_{11} = \frac{Y_{22}}{\Delta Y} = \frac{1}{6} \times \frac{18}{5} = \frac{3}{5}$$

$$\underline{\text{Because}} \quad \Delta Y = Y_{11}Y_{22} - Y_{12}Y_{21} = \frac{1}{18} + \frac{2}{9} = \frac{5}{18}$$

$$Z_{12} = \frac{-Y_{12}}{\Delta Y} = -\frac{2}{3} \times \frac{18}{5} = -\frac{12}{5}$$

$$Z_{21} = \frac{-Y_{21}}{\Delta Y} = \frac{1}{3} \times \frac{18}{5} = \frac{6}{5}$$

$$Z_{22} = \frac{Y_{11}}{\Delta Y} = \frac{1}{3} \times \frac{18}{5} = \frac{6}{5}$$

CONDITION FOR SYMMETRY :→

→ A two port network is said to be symmetrical if the ports can be interchanged without changing port voltages or currents.

(a) in terms of Z-parameter.

$$Z_{11} = Z_{22}$$

(b) in terms of Y-parameter.

$$Y_{11} = Y_{22}$$

(c) in terms of h-parameter.

$$\Delta h = 1 \quad \text{or} \quad \begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} = 1.$$

(d) in terms of ABCD parameters.

$$A = D.$$

CONDITION FOR RECIPROCITY :→

→ A network is said to be reciprocal if the ratio of the response to the excitation remains same to an interchange of the positions of the excitations and response in the network.

(a) in terms of Z-parameter.

$$Z_{12} = Z_{21}.$$

(b) in terms of  $\gamma$ -parameters.

$$\boxed{\gamma_{12} = \gamma_{21}}$$

(c) in terms of ' $h$ ' parameters.


$$\boxed{h_{12} = -h_{21}}$$

(d) in terms of ABCD parameters.

$$\boxed{\Delta T = 1.} \quad \text{or} \quad \boxed{AD - BC = 1.}$$

$$\text{or } \begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1.$$

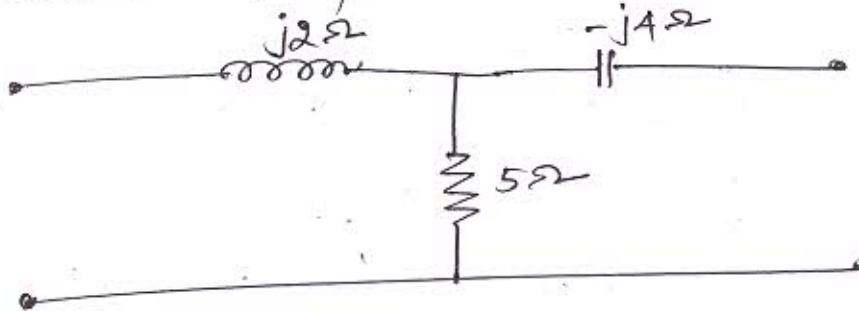
Example For the network shown in figure calculate T-parameters.



Solu<sup>n</sup> T-parameters equations are .

$$V_1 = A V_2 - B I_2 \quad (1)$$

$$I_1 = C V_2 - D I_2 \quad (2)$$

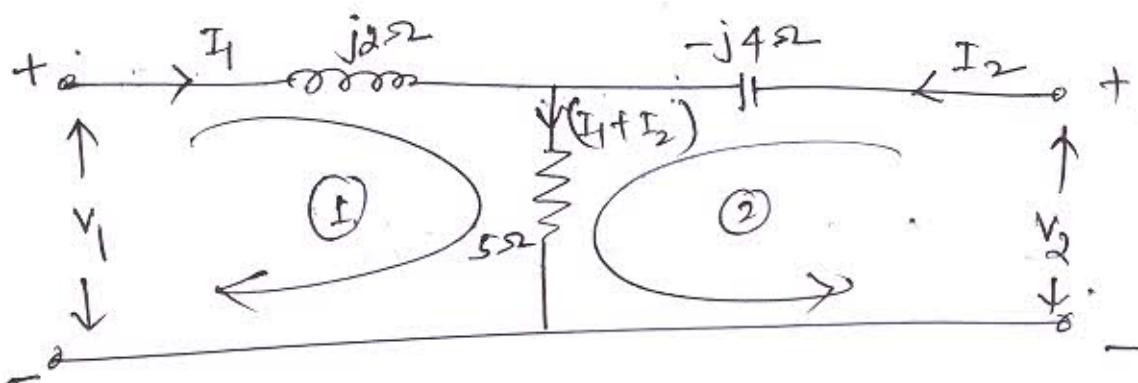

By KVL in Loop - (1)  $-j2s2 I_1 - 5(I_1 + I_2) + V_1 = 0$

$$\Rightarrow V_1 = (5+j2) I_1 + 5 I_2 \quad (3)$$

By KVL in Loop - (2)  $+j4 I_2 - 5(I_1 + I_2) + V_2 = 0$

$$\Rightarrow I_2 = 5 I_1 + (5-j4) I_2 \quad (4)$$

Putting  $I_1$  from equation (4) in equation (3)  
we get .

$$V_1 = (5+j2) \left[ \frac{V_2 - I_2(5-j4)}{5} \right] + 5 I_2$$

$$\Rightarrow V_1 = \left( \frac{5+j2}{5} \right) V_2 - \left[ \frac{(5+j2)(5-j4)}{5} - 5 \right] I_2 \quad (5)$$

For making as equation (2), rearrange equation.  
(A) we get.

$$I_1 = \frac{1}{5} V_2 - \left( \frac{5-j4}{5} \right) I_2 \quad \text{--- (6)}$$

To obtain T-parameters.  
Comparing eqn (1) and (5) we get.

$$A = \left( \frac{5+j2}{5} \right), \quad B = \frac{(5+j2)(5-j4)}{5} - 5 \\ = \left( \frac{8-j10}{5} \right)$$

Comparing equations (2) and (6) we get.

$$C = \left( \frac{1}{5} \right), \quad D = \left( \frac{5-j4}{5} \right)$$

Date - 04      24/04/2020


Page - 14

## INTERCONNECTIONS OF TWO PORT NETWORKS

- (1) Series connection
- (2) Cascade connection.
- (3) Parallel connection.
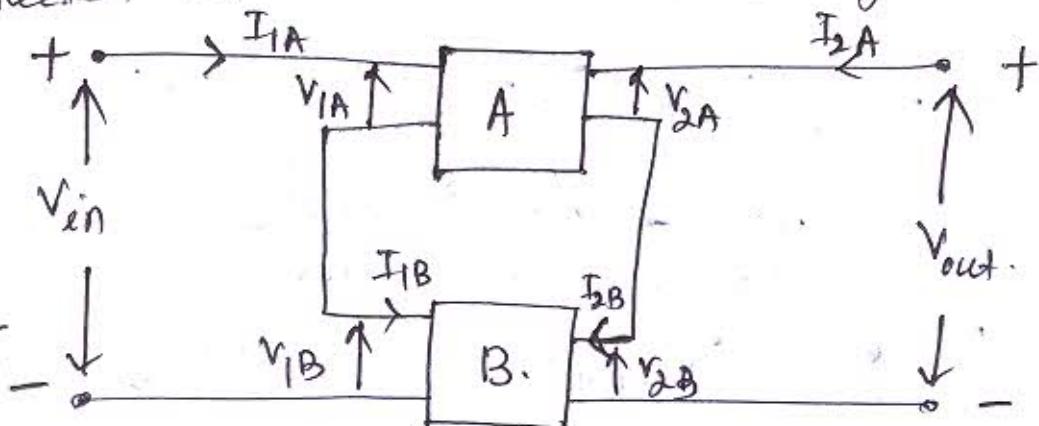
### (1) Series connection :-

Let network A and B be the two port networks connected in series as shown in figure.



(Series connection of two 2-port network)

For network A

$$V_{1A} = Z_{11A} I_{1A} + Z_{12A} I_{2A}$$

$$V_{2A} = Z_{21} I_{1A} + Z_{22A} I_{2A}$$

For network B

$$V_{1B} = Z_{11B} I_{1B} + Z_{12B} I_{2B}$$

$$V_{2B} = Z_{21B} I_{1B} + Z_{22B} I_{2B}$$

The interconnection results.

$$I_1 \equiv I_{1A} \equiv I_{1B} \quad \left| \quad V_1 = V_{1A} + V_{1B} \right.$$

$$I_2 \equiv I_{2A} \equiv I_{2B}$$

$$V_2 = V_{2A} + V_{2B}$$

$$V_1 = V_{1A} + V_{1B}$$

$$\Rightarrow V_1 = (z_{11A} I_{1A} + z_{12A} I_{2A}) + (z_{11B} I_{1B} + z_{12B} I_{2B})$$

$$\Rightarrow V_1 = I_1 (z_{11A} + z_{11B}) + I_2 (z_{12A} + z_{12B}) \quad \text{--- (1)}$$

And  $V_2 = V_{2A} + V_{2B}$

$$\Rightarrow V_2 = (z_{21A} I_{1A} + z_{22A} I_{2A}) + (z_{21B} I_{1B} + z_{22B} I_{2B})$$

$$\Rightarrow V_2 = I_1 (z_{21A} + z_{21B}) + I_2 (z_{22A} + z_{22B}) \quad \text{--- (2)}$$

Thus we get equn (1) and (2)  
in matrix form.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11A} + z_{11B} & z_{12A} + z_{12B} \\ z_{21A} + z_{21B} & z_{22A} + z_{22B} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Hence.  $[Z] = [Z_A] + [Z_B]$ .

Thus it has been observed that the overall Z-parameter matrix for series connected two port networks is simply the sum of Z matrices of each individual network.

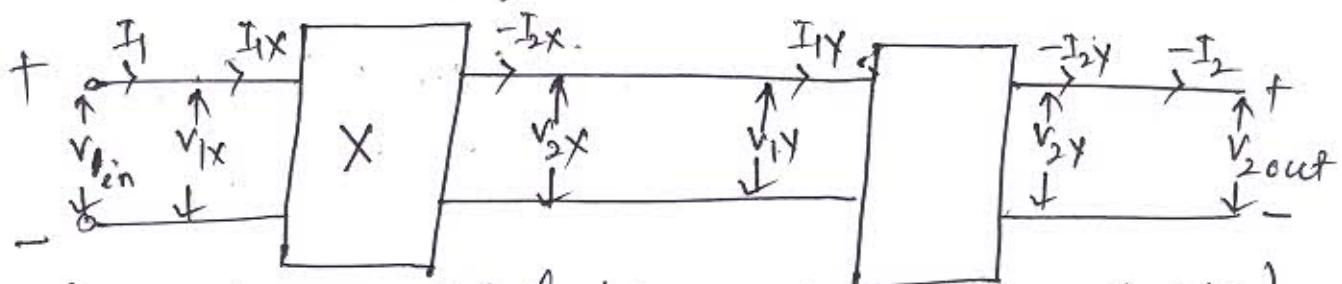(2) CASCADE CONNECTION  $\rightarrow$ 

$\rightarrow$  ABCD parameters are highly useful in characterising cascaded two port networks.

$\rightarrow$  Let  $X$  and  $Y$  be two networks connected in cascade.



(Cascade connected two numbers two port n/c)

For network X

$$v_{1X} = A_X v_{2X} - B_X I_{2X}$$

$$I_{1X} = C_X v_{2X} - D_X I_{2X}$$

For network Y

$$v_{1Y} = A_Y v_{2Y} - B_Y I_{2Y}$$

$$I_{1Y} = C_Y v_{2Y} - D_Y I_{2Y}$$

For the cascade connection

$$I_1 = I_{1X} ; -I_{2X} = I_{1Y} ; I_2 = I_{2Y}$$

$$v_1 = v_{1X} ; v_{2X} = v_{1Y} ; v_2 = v_{2Y}$$

The overall transmission parameters for the combined network as shown in fig (above) in matrix form —


$$\begin{aligned}
 \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} &= \begin{bmatrix} V_{1X} \\ I_{1X} \end{bmatrix} = \begin{bmatrix} Ax & Bx \\ Cx & Dx \end{bmatrix} \begin{bmatrix} V_{2X} \\ -I_{2X} \end{bmatrix} \\
 &= \begin{bmatrix} Ax & Bx \\ Cx & Dx \end{bmatrix} \begin{bmatrix} V_{1Y} \\ I_{1Y} \end{bmatrix} \\
 &= \begin{bmatrix} Ax & Bx \\ Cx & Dx \end{bmatrix} \begin{bmatrix} Ay & By \\ Cy & Dy \end{bmatrix} \begin{bmatrix} V_{2Y} \\ -I_{2Y} \end{bmatrix} \\
 &= \begin{bmatrix} Ax & Bx \\ Cx & Dx \end{bmatrix} \begin{bmatrix} Ay & By \\ Cy & Dy \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \\
 \Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} &= \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}
 \end{aligned}$$

whence.  $\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} Ax & Bx \\ Cx & Dx \end{bmatrix} \begin{bmatrix} Ay & By \\ Cy & Dy \end{bmatrix}$

The overall ABCD parameter network matrix for cascaded n/w is then the matrix product of ABCD matrices of individual n/w.
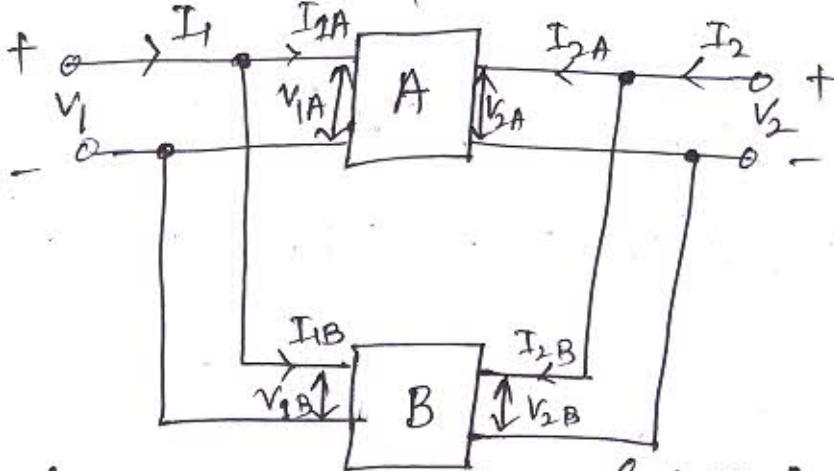
### (3) PARALLEL CONNECTION :

- Let A and B network be connected in parallel as shown in figure.
- $\gamma$ - parameter representation is very much useful.



(Parallel connection of two 2-port network)

For network A

$$I_{1A} = Y_{11A} V_{1A} + Y_{12A} V_{2A}$$

$$I_{2A} = Y_{21A} V_{1A} + Y_{22A} V_{2A}$$

For network B

$$I_{1B} = Y_{11B} V_{1B} + Y_{12B} V_{2B}$$

$$I_{2B} = Y_{21B} V_{1B} + Y_{22B} V_{2B}$$

For the parallel connection

$$V_1 = V_{1A} = V_{1B}, \quad V_2 = V_{2A} = V_{2B}$$

$$I_1 = I_{1A} + I_{1B}, \quad I_2 = I_{2A} + I_{2B}$$

$$\text{Thus } I_1 = I_{1A} + I_{1B}$$

$$\Rightarrow I_1 = (Y_{11A}V_{1A} + Y_{12A}V_{2A}) + (Y_{11B}V_{1B} + Y_{12B}V_{2B})$$

$$\Rightarrow I_1 = (Y_{11A} + Y_{11B})V_1 + (Y_{12A} + Y_{12B})V_2 \quad \text{--- (1)}$$

$$\text{And } I_2 = I_{2A} + I_{2B}$$

$$\Rightarrow I_2 = (Y_{21A}V_{1A} + Y_{22A}V_{2A}) + (Y_{21B}V_{1B} + Y_{22B}V_{2B})$$


$$\Rightarrow I_2 = (Y_{21A} + Y_{21B})V_1 + (Y_{22A} + Y_{22B})V_2 \quad \text{--- (2)}$$

Finally from eqn (1) and (2)  
in matrix form

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11A} + Y_{11B} & Y_{12A} + Y_{12B} \\ Y_{21A} + Y_{21B} & Y_{22A} + Y_{22B} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

\* The overall  $Y$  parameter matrix is then simply the summation of  $Y$  matrices of each individual two port network.

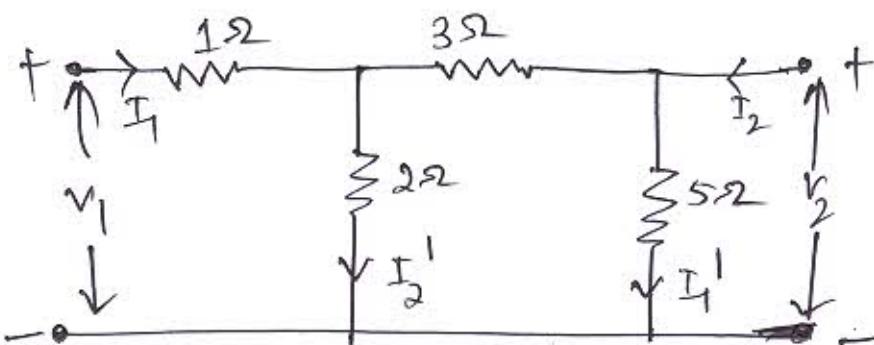Example. calculate the z-parameter in given fig.



Solu<sup>n</sup> case-I. ( $I_2 = 0$ )

$$Z_{11} = (8I_1) + 1 = \frac{16}{10} + 1 = \frac{16+10}{10} = 2.6\Omega$$

$$I_1' = \frac{2}{10} \times I_1 = \frac{I_1}{5}$$

$$V_2 = 5I_1' = 5 \times \frac{I_1}{5} = I_1$$

$$\Rightarrow Z_{21} = \frac{V_2}{I_1} = 1\Omega$$

Case - 2 ( $I_1 = 0$ )

$$Z_{22} = 5I_2 = \frac{5 \times 5}{5+5} = 2.5\Omega$$

$$I_2' = \frac{5}{10} I_2 = \frac{I_2}{2}$$

$$V_1 = 2I_2' = 2 \times \frac{I_2}{2} = I_2$$

$$Z_{12} = \frac{V_1}{I_2} = 1\Omega$$

Hence.

$$Z_{11} = 2.6\Omega, Z_{22} = 2.5\Omega$$

$$Z_{12} = Z_{21} = 1\Omega$$