

ROLL NUMBER

--	--	--	--	--	--	--	--	--	--

SRINIX COLLEGE OF ENGINEERING

SECOND INTERNAL EXAMINATION-2021-22

Subject-**BASIC ELECTRICAL ENGINEERING**

Semester-1st

Branch-**SEC-A**

Full Mark-**100**

Time-**2.30Hrs**

ANSWER ALL THE QUESTIONS (PART-A)

[2X10=20]

1. What is permeability?
2. Define Resistance and its unit.
3. Define peak factor.
4. How the power factor can be calculated by two wattmeter method.
5. Define phage voltage and phage current.
6. State thevenins theorem?
7. Convert polar to rectangular form $10 \angle 35^\circ$
8. Explain ohms law and mention the limitation of ohms law.
9. Define Biot savarts law.
10. Write down the EMF equation of DC motor.

ANSWER ANY EIGHT QUESTIONS (PART-B)

[6X8=48]

1. State and explain superposition theorem.
2. State difference between magnetic circuit and Electric circuit.
3. Explain the construction and principle of induction motor.
4. A generator supplies a variable frequency of voltage 150V in series RLC having $R=10\Omega$, $L=5\text{mH}$, $C=0.15\mu\text{F}$, find out inductive reactance, capacitive reactance, resonance frequency & voltage drop each element.
5. What is hysteresis loop; explain with the help of diagram.
6. State and explain Norton's theorem.
7. Explain self inductance and mutual inductance with suitable diagram
8. Explain different types of magnetic material
9. What is star and delta connection and convert star to delta connection.

ANSWER ANY TWO QUESTIONS (PART-C)

[16X2=32]

1. State and explain working principle of DC motor and explain different types of dc motor and its application different motor.
2. With a neat circuit and phasor diagram explain the 3-phase power measurement by 1-wattmeter method and 2-wattmeter method and also derive the expression for power factor..
3. (a) Define the venin theorem and explain in the steps with proper diagram.
(b) Discuss the principle and operation of 1-phase transformer and its types.