



REGISTRATION NUMBER

--	--	--	--	--	--	--	--	--	--

SRINIX COLLEGE OF ENGINEERING

2ND INTERNAL EXAMINATION-2021-22

Subject-BETC

Semester-1st

Branch- SEC-B

Full Mark-100

Time-2.30Hrs

ANSWER all QUESTIONS (PART-A)

[2X10=20]

- 1) (a) Distinguish between 3 different forms of matter in electronics.
- (b) What is diode? What is the application of diode and explain it?
- (c) What do you mean by OPAMP? Write its properties.
- (d) Convert $(133.6)_{10} = (?)_8$
- (e) Find the 2's compliment of $(110110)_2$ and $(26)_{10}$.
- (f) Differentiate between BJT and FET.
- (g) What is a MOSFET? What is the difference between D-MOSFET and E-MOSFET?
- (h) Write down the difference between combinational and sequential circuit
- (i) Find the relation between α and γ .
- (j) Define CMRR.

ANSWER ANY Eight QUESTIONS (PART-B)

[6×8=48]

- 1) Add (37) and (-57) in 2's compliment method.
- 2) Given $Y = A + B\bar{C}$. Find the standard SOP format and find the min terms.
- 3) Given $Y = \sum m(0,1,2,3,4,5,10,11,14,15)$. Solve using K-map.
- 4) Explain VI-characteristics of diode with diagram.
- 5) Explain the n-channel JFET with diagram.
- 6) Write a note on CMOS.
- 7) What do you mean by transistor configuration? Explain about CE configuration.
- 8) Describe about the non-inverting amplifier by using OPAMP.
- 9) Write a brief note Full Adder.
- 10) Explain about NPN transistor with diagram.

ANSWER ANY TWO QUESTIONS (PART-C)

[16×2=32]

- 1) Explain about various logic gates with relevant information.
- 2) Describe about D-MOSFET with its transfer characteristics curve.
- 3) Given $Y = A\bar{B} + C$
 - i) Draw using basic gates.
 - ii) Implement using only NAND gate
 - iii) Implement using only NOR gate.

-----ALL THE BEST-----