



REGISTRATION NUMBER

--	--	--	--	--	--	--	--	--

SRINIX COLLEGE OF ENGINEERING

1ST INTERNAL EXAMINATION-2021-22

Subject-DLD

Semester-3rd

Branch-CSE)

Full Mark-60

Time-2.00Hrs

ANSWER ALL QUESTIONS (PART-A)

[2X10=20]

1. Convert $(25.81)_{10} = (?)_2$.
2. Find the radix of $(\frac{42}{5})_r = (10)_r$.
3. Find the 2's complement of (i) 1101010 (ii) 0001010
4. Find $(1001101)_G$ to its binary format.
5. Write about XOR and NOR gate.
6. Write the absorption law and prove it?
7. Given $y = \sum m(0,1,3,5,7)$. Write its SOP forms?
8. Differentiate between combinational and sequential circuit.
9. Explain about 2x1 MUX.
10. Differentiate between synchronous and asynchronous counter.

ANSWER ALL QUESTIONS (PART-B)

[5X4=20]

1. Given $y = A\bar{B} + C$. Implement using (i) Basic gates (ii) NAND gates
2. A 7 bit Hamming code is $(1100110)_2$ Find the error bit and correct it.
3. Given $y = \sum m(0,1,3,6,10,11,14)$ Implement using (i) 4x1 MUX (ii) 8x1 MUX
4. Write the Demorgan's theorem and prove it ?

ANSWER ANY TWO QUESTION (PART-C)

[10x2=20]

1. Explain about ripple counter.
2. Convert SR to JK flip-flop.
3. Explain SISO?