

ROLL NUMBER

--	--	--	--	--	--	--	--	--	--

**SRINIX COLLEGE OF ENGINEERING**

3<sup>rd</sup> INTERNAL EXAMINATION-2021-22

Subject-DLD

Semester-3rd

Branch-CSE

Full Mark-100

Time-3.00Hrs

**ANSWER ALL THE QUESTIONS(PART-A)**

**[2X10=20]**

1. Convert  $(45.82)_{10} = (?)_2$ .
2. Find 1's compliment of  $(00101101)_2$  and  $(32)_{10}$
3. Write about OR and AND gate.
4. What are universal gates and why they are called so?
5. Given  $Y = ABC\bar{C} + ABC + \bar{A}BC + \bar{A}\bar{B}\bar{C}$ . Find the min-terms of the expression.
6. Explain about the half subtractor.
7. What do you mean by a MUX, write with example.
8. Write down the characteristics table of SR and JK flip-flop.
9. Differentiate between Latch and Flip-flop.
10. Define counter and write its application.

**ANSWER ALL THE QUESTIONS (PART-B)**

**[6X8=48]**

1. By using the 2's compliment addition method perform the addition of  $-(32)_{10}$  and  $-(15)_{10}$
2. A 7 bit Hamming code is obtained as  $(1101011)_2$ . Find the error bit and writes the correct code.
3.  $Y = \bar{A}B + C(A \oplus B)$ . Draw this expression by using basic gates.
4. Given  $Y = (A + \bar{B})(A + C)$ . Find the standard POS form and write its max-terms.
5. Write a note on 4x1 MUX.
6. Explain JK flip-flop with diagram.
7. Convert SR flip-flop to D flip-flop with diagram.
8. Explain SISO shift register.

**ANSWER ALL THE QUESTIONS (PART-C)**

**[16X2=32]**

1. Define a logic gate. Explain about the logic gates with their relevant information.
2. Given  $Y = \sum M(0,1,3,4,6,9,11,12,15)$  implement this expression using
  - (i) 4x1 MUX
  - (ii) 2x1 MUX