

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
PEE3I103

3rd Semester Regular / Back Examination 2018-19

ELECTRICAL MACHINES – I

BRANCH : ELECTRICAL

Time : 3 Hours

Max Marks : 100

Q.CODE : E933

Answer Question No.1 (Part-1) which is compulsory, any EIGHT from Part-II and any TWO from Part-III.

The figures in the right hand margin indicate marks.

Part- I

Q1 Short Answer Type Questions (Answer All-10)

(2 x 10)

- Classify the AC machines?
- Draw the phasor diagram for a practical transformer with lagging power factor load.
- What do understand by an ideal transformer?
- Explain why the primary mmf must be equal and opposite to the secondary mmf in an ideal transformer.
- Why per unit system of measurement is required in machine performance analysis?
- What is main drawback of an autotransformer as compared to an ordinary transformer? What is the application of auto transformer?
- How third harmonic component in a power transformer can be eliminated without filter circuit?
- A 208-V, 60-Hz, 4-pole, three-phase induction motor has a full-load speed of 1755 rpm. Calculate (a) its synchronous speed, (b) the slip, and (c) the rotor frequency.
- Explain why an induction motor cannot operate at its synchronous speed.
- What would happen If the rotor of the induction motor is driven faster than synchronous speed? Draw the torque-speed characteristic showing the statement.

Part- II

Q2 Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve)

(6 x 8)

- The magnetization current in a practical transformer is not sinusoidal. Explain the statement with waveform.
- Draw and explain the exact and approximate equivalent circuit of a transformer.
- The available power out of the open-delta bank is only 57.7 percent of the original bank's rating. Justify.
- Draw the experimental set-up for open and short circuit test of single phase transformer.
- A 2000/200 V, 20kVA transformer is connected as a step-up auto-transformer (2000/2200V). Calculate its kVA rating, kVA transferred inductively, conductively and its efficiency at full load 0.8 p.f.
- Describe the no-load test, blocked-rotor test of an induction motor.
- Draw the flow diagram for power input to output including losses at various stages of the three phase induction motor.
- Discuss about the crawling and cogging of induction motor.
- Draw the experimental set-up of a back-to back connection of two single phase transformers. Why this is done so?
- Derive the expression for copper saving of an auto-transformer as compared to ordinary transformer of same rating.
- Develop the criteria for the maximum torque developed by induction motor during running.
- Discuss the double field revolving theory. Draw the equivalent circuit for a single-phase induction motor considering both forward and backward rotor branches at rest.