

h) The type of single-phase induction motor having the highest power factor at full load is

- (A) shaded pole type (B) split-phase type
(C) capacitor-start type (D) capacitor-run type

i) It is desired to measure parameters of 230 V/115 V, 2 kVA, single-phase transformer. The following wattmeters are available in laboratory:

- W1 : 250 V, 10 A, Low Power Factor W2 : 250 V, 5 A, Low Power Factor
W3 : 150 V, 10 A, High Power Factor W4 : 150 V, 5 A, High Power Factor

The Wattmeters used in open circuit test and short circuit test of the transformer will respectively be

- (A) W1 and W2 (B) W2 and W4 (C) W1 and W4 (D) W2 and W3

j) The direction of rotation of a 3-phase induction motor is clockwise when it is supplied with 3-phase sinusoidal voltage having phase sequence A-B-C. For counter clockwise rotation of the motor, the phase sequence of the power supply should be

- (A) B-C-A (B) C-A-B (C) A-C-B (D) B-C-A or C-A-B

Q2 Answer the following questions:

(2 x 10)

- Why the voltage regulation of a transformer is zero or negative for leading power factor load?
- A single phase transformer has a hysteresis and eddy current loss of 150W and 100W respectively when supplied from 250V, 50Hz. What will be the corresponding losses when supplied from 220V, 30Hz?
- Draw the phasor diagram of a transformer supplying power at full load 0.8 leading power factor.
- A 3-phase I.M. has slots/pole/phase=5. If the coil span=13 slots, determine the winding factor.
- Explain the advantage of using tertiary winding in 3 phase transformer?
- Three single phase transformer connected in Dd0, delivering full load, if one of the transformer is taken out of operation, find the % overloading of each transformer?
- Explain why an induction motor at no load operates at a very low power factor?
- Why you need a starter to start a poly phase induction motor?
- Draw the torque slip characteristics of a single phase Induction motor?
- Explain how the speed of a single phase induction motor can be controlled?

Part - B (Answer any four questions)

- Q3 a)** A 5KVA, 2200/220 V, single phase transformer has the following parameters $R_1=3.4\Omega$, $R_2=0.028\Omega$, $X_1=7.2\Omega$ and $X_2=0.06\Omega$. Determine
a) the input current and power factor, b) Terminal voltage when a load of $4+j5\Omega$ is connected (c) Equivalent circuit refer to both side. (10)
- b) Derive the expression for voltage regulation for a single phase transformer. (5)