

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 03

B.Tech
PEE3I101 / PEI3I104 / PEL3I101 / PET3I102

3rd Semester Back Examination: 2021-22

NETWORK THEORY

BRANCH(S): ELECTRICAL / AEIE, EIE / EEE, ECE / ETC

Time : 3 Hour

Max Marks : 100

Q.Code : OF608

Answer Question No.1 (Part-1) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

Part-I

Q1 Answer the following questions : (2×10)

- State Tellegen theorem.
- For a circuit with $R=4\ \Omega$, $L=25\text{mH}$, $C=150\ \mu\text{F}$ in series. Calculate the band width.
- The Z-parameters of a two-port network are given as $Z_{11}=5\ \Omega$, $Z_{22}=7\ \Omega$, $Z_{12}=Z_{21}=3\ \Omega$. Find the A,B,C,D parameters.
- State initial and final value theorem.
- Prove that the efficiency of maximum power transfer theorem is 50%. Determine h-parameters, in terms of given Y -parameters $Y = \begin{bmatrix} 0.1 & 0.1 \\ 0.4 & 0.5 \end{bmatrix}$
- Write down the properties of series RC impedance function.
- State Superposition theorem with an example.
- Test the polynomial $2s^4 + 5s^3 + 6s^2 + 3s + 1$ for Hurwitz character.
- Find the equivalent inductance across the input terminals of Fig.1, having $L_1 = 1\ \text{H}$, $L_2 = 2\ \text{H}$ and $M = 0.5\ \text{H}$

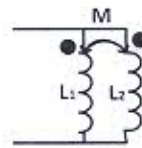


Fig.1

Part-II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6×8)

- Apply Millman's theorem to find the current in the load resistor ($R_L = 5\ \Omega$) in the circuit shown in Fig.2.

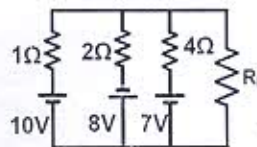


Fig.2

- Draw the pole-zero diagram of the given function $V(s)$ and determine

$$v(t).V(s) = \frac{4s}{(s+2)(s^2+2s+2)}$$

- c) Derive the condition for reciprocity and symmetry in terms of ABCD parameters for a 2-port network.
- d) What is Initial value theorem and Final Value Theorem? Also find the initial and final value of the function $f(t)$, whose Laplace Transform is given as $\frac{4s}{(s+2)(s^2+2s+2)}$
- e) Find the trigonometric Fourier series of the waveform shown in Fig. 3. Draw the magnitude and phase spectrum.

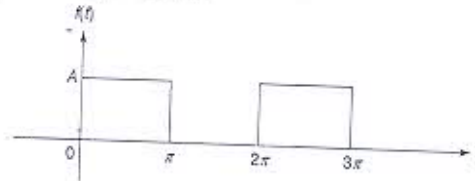


Fig.3

- f) A resistor and a capacitor are in series with a variable inductor when the circuit is connected to a 200 V, 50 Hz supply, the maximum current obtained by varying the inductance is 0.314 A. The voltage across the capacitor is then 300 V. find the circuit constants?
- g) Check whether the following function is positive real or not.
- $$F(S) = \frac{S^2 + 10S + 4}{S + 2}$$
- h) Design a constant K band pass filter with cut off frequencies of 3KHZ and 7.5 KHZ and nominal characteristic impedance of 900 Ω.
- i) A circuit consists of a non inductive resistor of 10 Ω, an inductor of 0.1H and capacitor of 8μF in series. Calculate (a) the resonant frequency (b) current at resonant frequency (c) the voltage across each component when a voltage of 25V at resonant frequency is applied to the whole circuit.
- j) In the network of Fig.4 shown, the switch is moved from the position 1 to 2 at $t = 0$, steady-state condition having been established in the position 1. Determine $i(t)$ for $t > 0$.

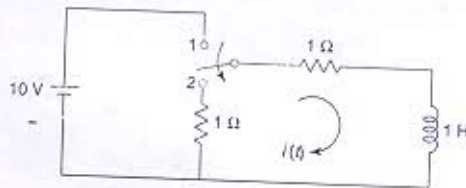


Fig.4

- k) Using superposition theorem determine the voltage across the $(2 + j5)$ ohm impedance for the network shown in Fig.5.

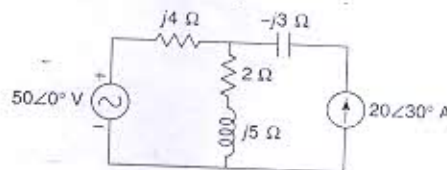


Fig.5

- l) Two impedances $Z_1 = 20 + j10$ and $Z_2 = 10 - j30$ are connected in parallel and this combination is connected in series with $Z_3 = 30 + jX$. Find the value of X

$$\omega_0 = \frac{2\pi f}{T} = \frac{2\pi}{T}$$