

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
RBE2B001

2nd Semester Regular Examination 2018-19
BASIC ELECTRICAL ENGINEERING
BRANCH : AEIE, AG, AUTO, BIOMED,
BIOTECH, CHEM, CIVIL, CSE, ECE, EEE, EIE, ELECTRICAL,
ETC, IT, MECH, METTA, MINING, MME, PE, PT

Max Marks : 100

Time : 3 Hours

Q.CODE : F357

Answer Question No.1 (Part-1) which is compulsory, any EIGHT from Part-II and any TWO from Part-III.

The figures in the right hand margin indicate marks.

Part- I


Q1 Only Short Answer Type Questions (Answer All-10) (2 x 10)

- What is the approximate resistance of a rheostat if the voltage source is 12 V and the current is 220 mA?
- A certain circuit is composed of two parallel resistors. The total resistance is $1,403\Omega$. One of the resistor is $2\text{ k}\Omega$. The other resistor value is?
- State the venin's theorem.
- Define RMS voltage.
- Represent the vector $5+j10$
- State Biotsavart slaw.
- If the cross-sectional area of a magnetic field increases, but the flux remains the same, the flux density _____.
- The voltage across a coil when $di/dt = 20\text{ mA}/\mu\text{ s}$ and $L = 8\ \mu\text{ H}$ is _____.
- Why the efficiency of the transformer is maximum among all electrical machines/Devices.
- Write the EMF equation of D.C generator.

Part- II


Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- a) Find the R_{AB} in the circuit.

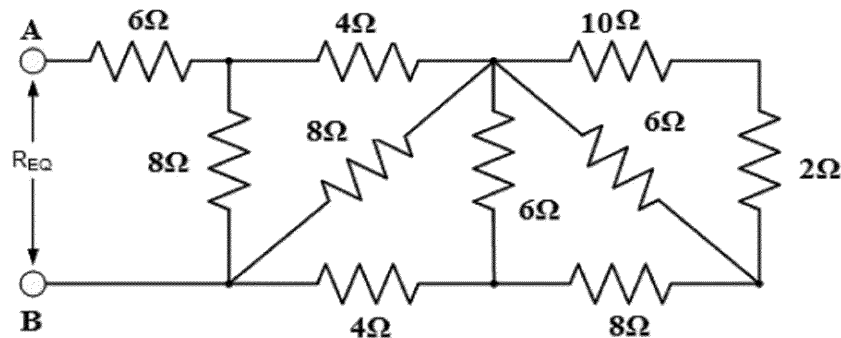


- b) Explain B-H curve for magnetic and formulate hysteresis.

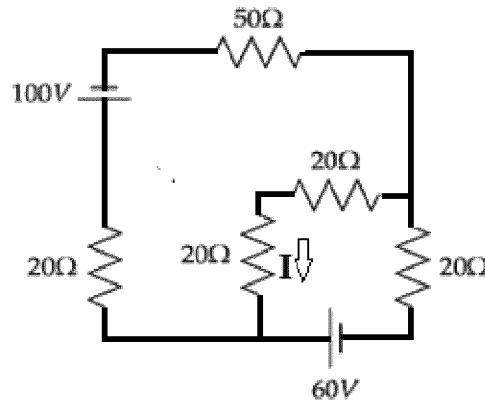- c) Find the value of I using superposition theorem.



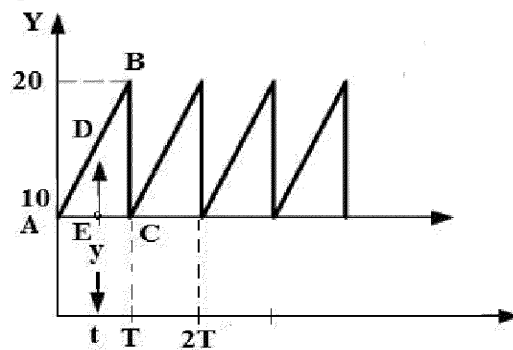- d) Determine R.M.S and average value of the wave form shown?



- e) A square wave has frequency of 50Hz and peak value of 12 Amp. Calculate the Average value, Peak factor and form factor.
- f) State and explain Norton's theorem with suitable example.
- g) An iron ring wound with 550 turns solenoid produces a flux density of 0.94 tesla in the ring carrying a current of 2.4 Amp. The mean length of iron path is 80 cm and that of air gap is 1 mm. Determine the relative permeability of iron and self-inductance.
- h) An alternating current is given by $i = 14.14 \sin 377 t$. Find R.M.S Value, frequency and sketch the waveform.
- i) Write the principle of DC Generator and derive the EMF equation.
- j) Give the comparison between Electric and magnetic Circuit.
- k) Explain the construction and principle of three phase induction motor.
- l) The armature of a 6-pole, 600 RPM lap-wound generator has 90 slots. If each coil has 4 turns, calculate the flux per pole required to generate an EMF of 288 Volts.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

- Q3** Explain the conversion process of star network to a delta network and vice versa and write the voltage and current relations in star and delta network. (16)
- Q4** Discuss the principle of operation and testing of single phase transformer. Draw the Phasor diagram. (16)
- Q5** With a neat circuit and Phasor diagram explain the three phase power measurement by two wattmeter method and also derive the expression for Power Factor. (16)
- Q6** A series RLC circuit has $R=20 \text{ ohm}$, $L=0.005\text{H}$ and $C = 0.2 \times 10^{-6}\text{F}$. It is fed from a 100V variable frequency source. Find (16)
- frequency at which current is maximum
 - Impedance at this frequency and
 - Voltage across inductance at this frequency.