

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
BE2101

2nd Semester Back Examination 2018-19

BASIC ELECTRONICS

BRANCH : CHEM, CIVIL, CSE, ECE, EEE, ELECTRICAL, IT, MECH

Time : 3 Hours

Max Marks : 70

Q.CODE : F112

Answer Question No.1 which is compulsory and any FIVE from the rest.

The figures in the right hand margin indicate marks.

- Q1 Answer the following questions : (2 x 10)**
- a) What do you mean by break region of a diode?
 - b) Why the gain of an amplifier reduces at very high and very low frequency?
 - c) State and explain Bark-Hausen criterion.
 - d) What is the difference between combinational and sequential circuit?
 - e) Why common collector configuration is called an emitter follower circuit? Comment.
 - f) Write down the relationship between I_{CO} and I_{CEO} .
 - g) Compare the advantages and disadvantages between center-tapped and bridge type full wave rectifier.
 - h) What is the relationship between the period of a waveform and its frequency?
 - i) What do you mean by digital logic invertors? Mention two ICs used as digital logic invertors.
 - j) Define CMRR and Slew rate of an Op-Amp. Mention its significance.
- Q2 a) What is Lissajous method? Does Lissajous method require sweep signal? State and explain the function of the sweep signal in an oscilloscope. Justify the answer with a suitable block diagram or graph. (5)**
- b) Draw a crystal controlled oscillator circuit. Also state its advantages and disadvantages. (5)**
- Q3 a) Draw and explain a small signal high frequency CE model of a transistor. (5)**
- b) Explain the operation of a full wave bridge rectifier with its input and output waveforms. (5)**
- Q4 a) What do you mean by binary number system? What are the advantages of actual and Hexadecimal number systems and which system is used most commonly? (5)**
- b) How the transistor can be used as an amplifier in CE configuration? Explain with proper diagram. (5)**

- Q5** a) What is a signal generator? Explain the operation of a signal generator with a neat block diagram. **(5)**
b) Differentiate between static and dynamic RAM. **(5)**
- Q6** Implement a full adder circuit using two 4:1 multiplexers. **(10)**
- Q7** Draw and explain the circuit of a basic differentiator. What are the limitation of this circuit and how these are overcome in practical differentiator circuit? **(10)**
- Q8** **Write short answer on any TWO :** **(5 x 2)**
a) Small signal analysis.
b) Feedback amplifier.
c) AF signal generator.