

STUDY MATERIAL

SUBJECT : BASIC ELECTRICAL ENGG. (BEE)
(MODULE - I)

Soc-B

SEMESTER : 1ST / 2ND

BRANCH : MECH/CE/EE/EEE/CSE/ETC

Sem 2nd
BEE

DEPARTMENT OF ELECTRICAL ENGINEERING
SRINIX COLLEGE OF ENGINEERING, BALASORE
(www.srinix.org)

Electric charge

Atom consist of electrons, protons & neutrons.

- Electron has -vely charge ($-1.6 \times 10^{-19} \text{ C}$)
- Proton has +vely charge ($1.6 \times 10^{-19} \text{ C}$)
- Neutron has no charge.
- Study of charge is called Electricity

Electric current
An Electric current is the movement of electric charge along a definite path.

- In case of conductor moving of ~~electron~~ charges are electron.
- Unit is Ampere.

$$\boxed{I = \frac{Q}{t}} \quad \text{or} \quad \boxed{Q = It}$$

Steady current

(a) Direct current :- it is a current whose magnitude as well as direction remain constant.

→ Ex - cell, battery, dc generator.

(b) Alternating current :- it is the current whose magnitude & direction changes regular interval of time.

(c) Varying current :- the current whose magnitude change but direction unchanged



Q. 2.7
(c) starting Transient current
It is a current for a very short interval of time.

Ex:- In ckt Concept of Capacitor

emf The force which causes the flow of electron is called emf.

→ force is nothing but energy experience on the charges.

$$E = \frac{W}{Q} \rightarrow \begin{array}{l} \text{energy experience (Joules)} \\ \text{charge transferred in} \\ \text{Coulombs} \end{array}$$

$E \rightarrow$ emf of source.

voltage Energy would be required if a charge transferred from one point to another ckt.

→ Energy required movement of charge from one ckt to another

$$V = \frac{W}{Q}$$

Resistance The properties of material which oppose the flow of current.

→ Unit is Ω (ohm)
Conductance - Reciprocal of Resistance (Siemen)
Unit is Siemen

Specific Resistance & Resistivity (ρ)

Conductivity - ~~reciprocal of resistivity~~

Resistance of the Conductor is directly length of Conductor & Inversely proportional to the crosssectional area of the Conductor.

$$R \propto \frac{l}{A} \Rightarrow R = \frac{\rho l}{A}$$

i.e. $R \propto \frac{l}{A} \Rightarrow R = \frac{\rho l}{A}$
 $\left[\rho = \frac{RA}{l} \right] \rightarrow$ specific resistance.

Conductivity :- It is Reciprocal of Resistivity

$$\sigma = \frac{1}{\rho}$$

$\sigma \rightarrow$ conductivity
Unit Siemens/meter

Ohm's law

Ohm's law states that the current through any conductor is directly proportional to potential difference between its ends

$$I \propto V$$


$$I = \frac{1}{R} \cdot V \Rightarrow \boxed{V = RI}$$

Circuit :- A circuit is a closed path through which electric current passes through it.

Node :- Node is a junction in a circuit where two or more circuit elements are connected together. $\rightarrow$ node.

Branch

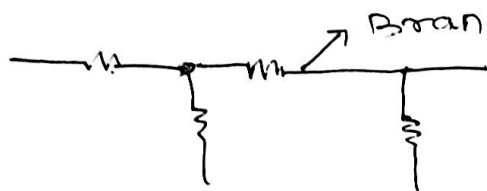Branch is a part of network which lies between two junctions.



Loop

It is a closed path in a circuit in which no element or node is encountered more than once.


A path ^{or} which contains more than two mesh is called loop.

Mesh

Any path which contains no other paths within it is called mesh.

Here



6 nodes

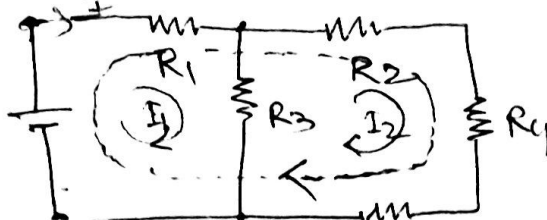




Here 2 mesh
3-loop

BASIC ELECTRICAL ENGG


SIGN CONVERSION

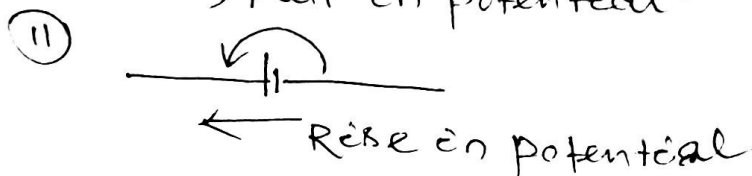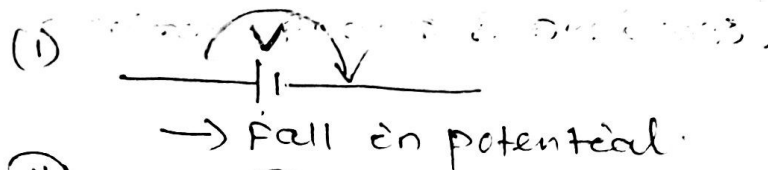

Convert
voltage source → current source

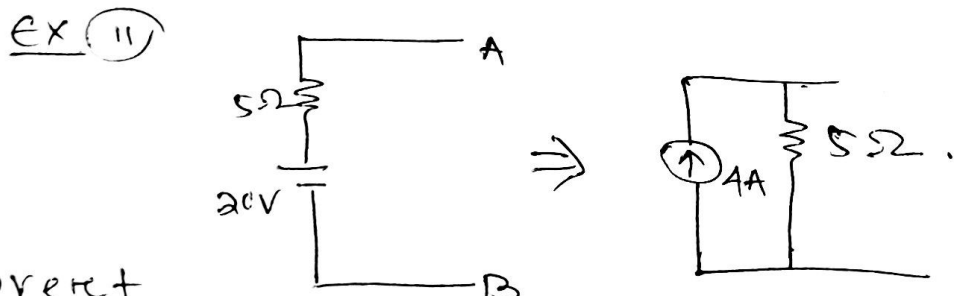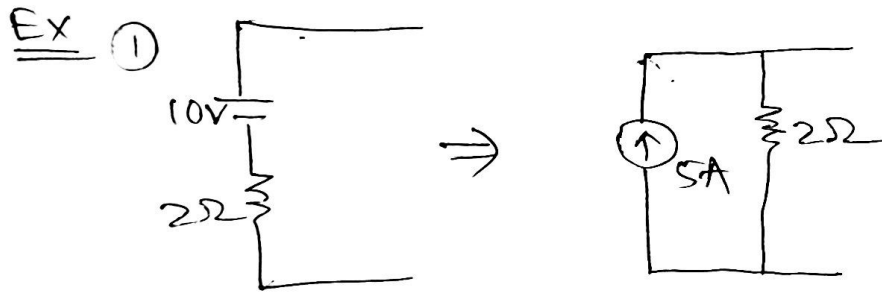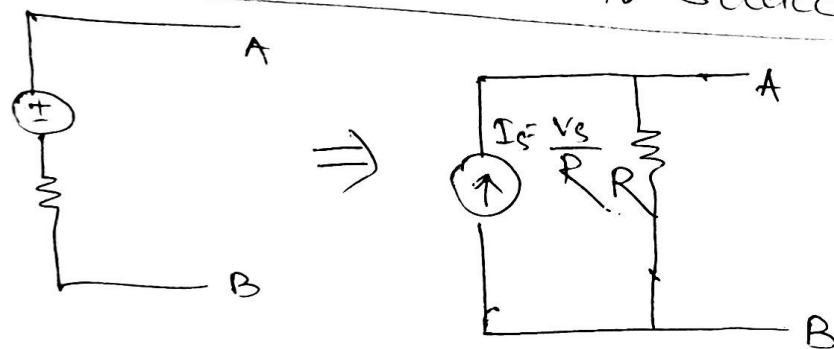

Convert
current source to voltage source

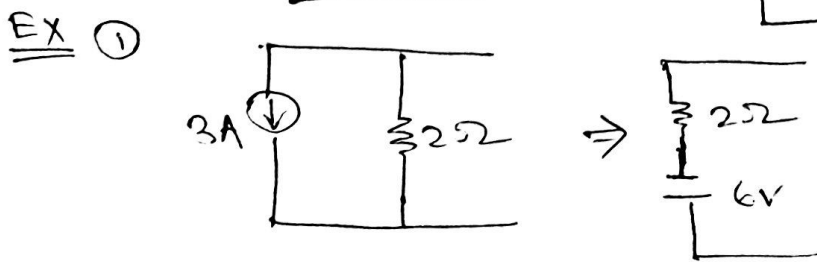

Kirchoff's law


Basically Kirchoff's ~~two~~ two laws

(1) Kirchoff's current law.

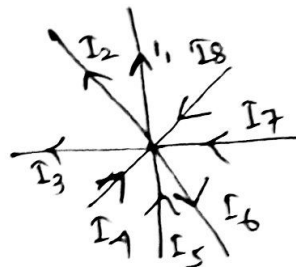(2) Kirchoff's voltage law

Kirchoff's current law

The Algebraic sum of current meeting at any junction in an electric ckt is zero.



$$I_1 + I_2 + I_3 + I_6 = I_8 + I_7 + I_4 + I_5$$


$$I_1 + I_2 + I_3 + I_6 - (I_8) - (I_7) - (I_4) - (I_5) = 0$$

$$\boxed{\sum I = 0}$$

Kirchoff's voltage law

In any closed ckt, the algebraic sum of the emf's and the sum of the product of current & resistance of each part of the ckt is equal to zero.

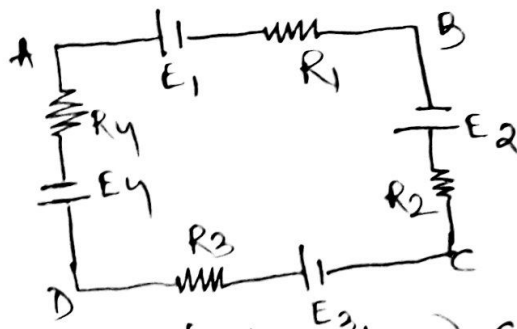Mathematically $\sum IR + \sum \text{emf} = 0.$




Apply KVL to the closed ckt ABCD.

$$-E_1 - IR_1 + E_2 - IR_2 + E_3 - IR_3 - E_4 - IR_4 = 0$$

problem

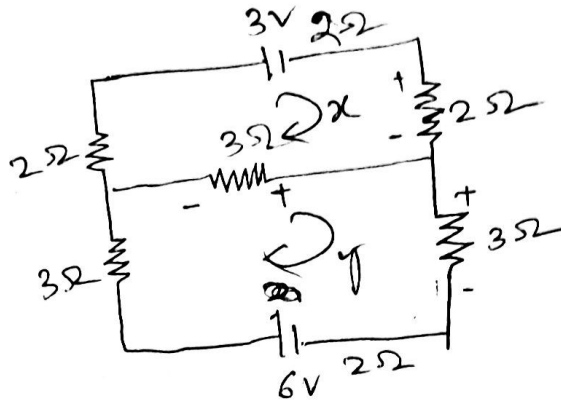(1) By applying mesh analysis, find p.d across AB.



Soln mesh-01

$$-2x - 2x - 3 - 2x - 3(x-y) = 0$$

$$-9x + 3y = 3$$

$$y = 3x + 1 \quad \text{--- (1)}$$

mesh-02

$$-3(y-x) - 3y + 6 - 3y - 2y = 0$$

$$-11y + 3x = -6$$

$$11y - 3x = 6 \quad \text{--- (2)}$$

Putting the value of y in eqn (2)

$$11(3x+1) - 3x = 6$$

$$x = \frac{-5}{30} = -\frac{1}{6} \text{ Amp.}$$

$$y = 3x + 1 = 3\left(-\frac{1}{6}\right) + 1 = \frac{1}{2}$$


$$\text{current AB} = \frac{1}{6} + \frac{1}{2} = \frac{2}{3} \text{ A}$$

$$\text{p.d across AB} = 3 \times \frac{2}{3}$$


$$= 2 \text{ Volt.}$$

Superposition Theorem

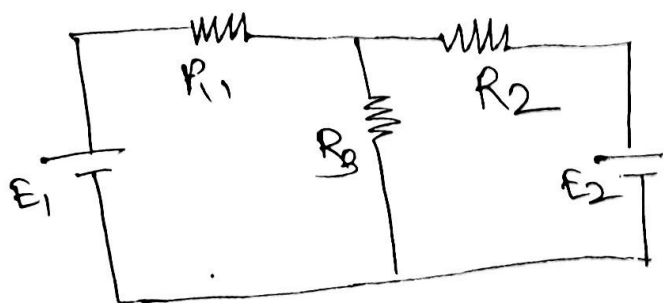Statement:- In a linear bilateral N/w containing more than one energy source, the resultant current in any branch is the algebraic sum of the currents that would be provided by each energy source acting alone.



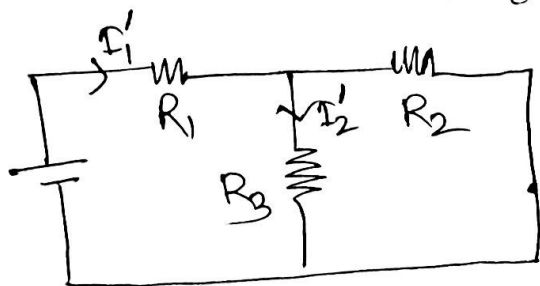Step-01 Consider the voltage source E_1 & source E_2 is short circuited



Let I_1' current from E_1

$$I_1' = \frac{E_1}{R_{eq}} = \frac{E_1}{(R_2 \parallel R_3) + R_1} \quad \text{--- (1)}$$

$$\begin{aligned} R_{eq} &= (R_2 \parallel R_3) + R_1 \\ &= \left(\frac{R_2 R_3}{R_2 + R_3} \right) + R_1 \\ R_{eq} &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_3} \quad \text{--- (2)} \end{aligned}$$

Putting this value in eqn (1)

$$I_1' = \frac{E_1 (R_2 + R_3)}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$


$$I_2' = I_1' \left\{ \frac{R_2}{R_2 + R_3} \right\}$$

$$I_2' = \frac{E_1 (R_2 + R_3)}{R_1 R_2 + R_2 R_3 + R_3 R_1} \times \frac{R_2}{R_2 + R_3}$$

Putting the value of I_1'

$$I_2' = \frac{E_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

Step-02

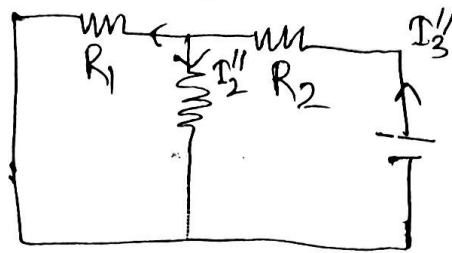

$$I_3'' = \frac{E_2}{R_{eq}}$$

$$R_{eq} = (R_1 \parallel R_3) + R_2 = \left(\frac{R_1 R_3}{R_1 + R_3} \right) + R_2$$

$$= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_3}$$

Putting the value in eqn (*)

$$I_3'' = \frac{E_2 (R_1 + R_3)}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$


$$I_2'' = I_3'' \left\{ \frac{R_1}{R_1 + R_3} \right\}$$

$$= \frac{E_2 (R_1 + R_3)}{R_1 R_2 + R_2 R_3 + R_3 R_1} \times \frac{R_1}{(R_1 + R_3)}$$


$$I_2'' = \frac{E_2 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$\text{Total current} = I_2' + I_2''$$

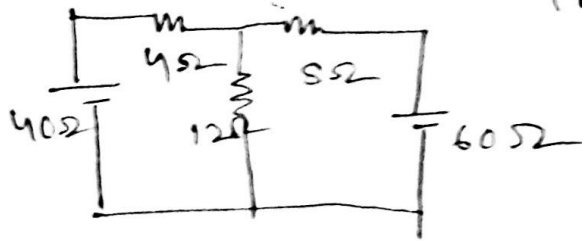Problem (SPT) Find the current in 12Ω Resistor in the ckt using SPT.



Step-1

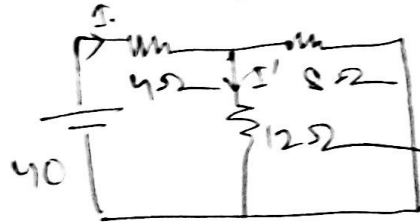


$$I = \frac{V}{R_{eq}} = \frac{40}{(12 \parallel 8) + 4} = \frac{50}{11} \text{ A.}$$

$$I' = \frac{50}{11} \left\{ \frac{8}{12+8} \right\}$$

$$= \frac{20}{11}$$

Step-02

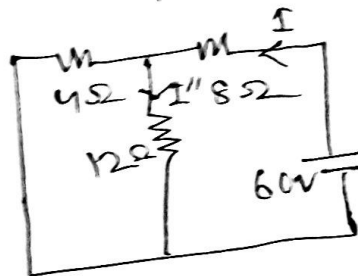

$$I = \frac{60}{(12 \parallel 4) + 8} = \frac{60}{11} \text{ Amp.}$$

$$I'' = I \left\{ \frac{4}{12+4} \right\}$$

$$= \frac{60}{11} \left\{ \frac{4}{16} \right\}$$

$$= \frac{15}{11} \text{ Amp.}$$


Hence total current

$$I = \frac{20}{11} + \frac{15}{11} = \frac{35}{11} = 3.19 \text{ Amp.}$$


Thevenin's Theorem

Any linear active (DC) N/w can be represented by an equivalent source called as Thevenin's Voltage, (V_{TH})

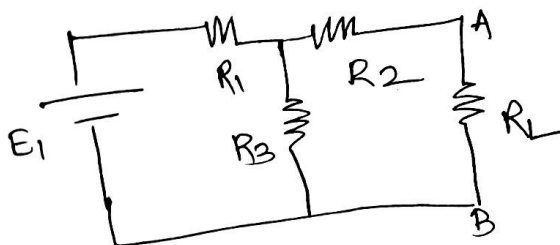Which is obtained by openct the load Resistance and another series resistance is Thevenin equivalent Resistance (R_{TH}) will be added to it. This Resistance being the Internal Resistance of that looking from openct (OC) load terminal.



Step-1

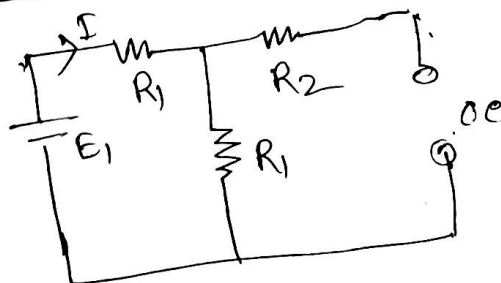

$$I = \frac{E_1}{R_1 + R_3}$$

$$V_{TH} = I R_3$$

$$= \left(\frac{E_1}{R_1 + R_3} \right) R_3 = \frac{E_1 R_3}{R_1 + R_3}$$


$$V_{TH} = \frac{E_1 R_3}{R_1 + R_3}$$

Step-02

R_{TH} found looking from the O.C load Resistance.
Replacing the Battery source.

Soln :-

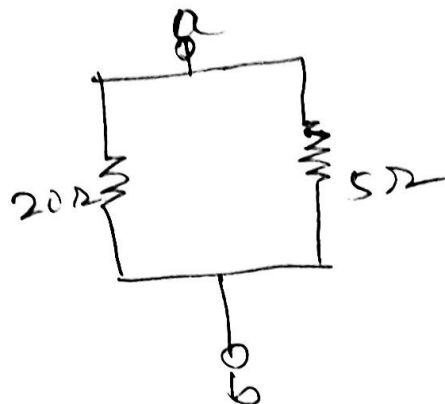
on replacing voltage source by zero internal Resistance & removing R_L



$$R_{TH} = (5 \parallel 20) = \frac{5 \times 20}{5 + 20} = 4 \Omega.$$

Calculation V_{TH}

on removing R_L we get.

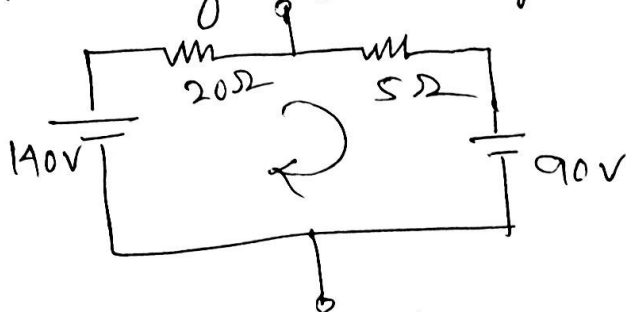

Applying KVL we get

$$-20I - 5I - 90 + 140 = 0.$$

$$-25I = -50 \Rightarrow \boxed{I = 2A}$$

$$V_{TH} = \text{p.d across a and b}$$


$$= 140 - 20I$$

$$= 140 - 20 \times 2 = 100V$$

$$I = \frac{V_{TH}}{R_{TH} + R_L}$$


$$= \frac{100}{4 + 10} = \frac{100}{14} = 7.14A.$$
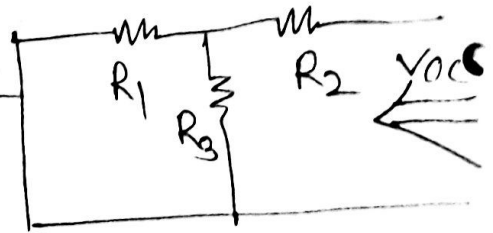
$$\begin{aligned}
 R_{TH} &= (R_1 \parallel R_3) + R_2 \\
 &= \left(\frac{R_1 R_3}{R_1 + R_3} \right) + R_2 \\
 &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_3}
 \end{aligned}$$




Step-03

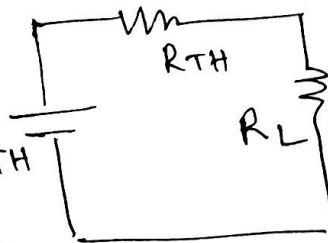Now Thevenin's V_{TH} equivalent ckt to be drawn as fig.



$$I_x = \frac{V_{TH}}{R_{TH} + R_L}$$

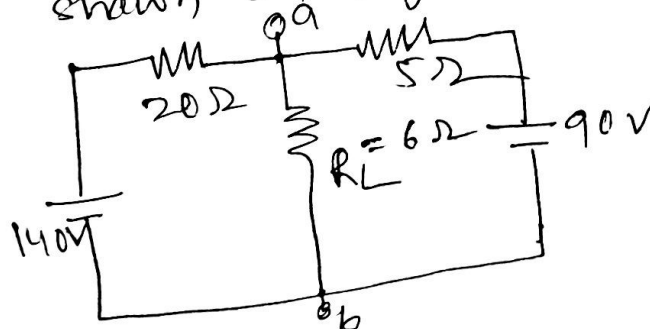Problem :- Using Thevenin's theorem determine the value of current in load resistance $R_L = 6\Omega$ as shown in fig.



A.C. Theory

(AC) Alternating Current :- Alternating current is that current which alters both in value & direction periodically it is denoted as a.c

→ This current increase from zero to max. value & then decreases from zero to max. value & then decrease to zero. in one direction.


$\rightarrow$ $g + i\omega$ Symbolically represent by $\odot \sim$
 $\rightarrow$ AC Can be ~~convert~~ converted by Rectifier
DC :- Direct Current

It is a current which always flow in one direction it is known as continuous current or Unidirectional current

→ It is denoted as d.c

→ $g + i$ found from battery cell.

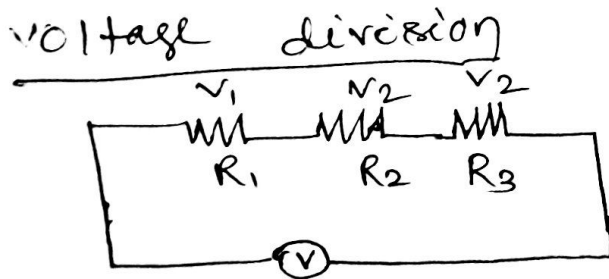→ DC can be converted into AC by inverter.




$$R_{eq} = R_1 + R_2 + R_3$$

$$V_1 = V \left\{ \frac{R_1}{R_1 + R_2 + R_3} \right\}$$

$$V_2 = V \left\{ \frac{R_2}{R_1 + R_2 + R_3} \right\}$$

$$V_3 = V \left\{ \frac{R_3}{R_1 + R_2 + R_3} \right\}$$

Current division

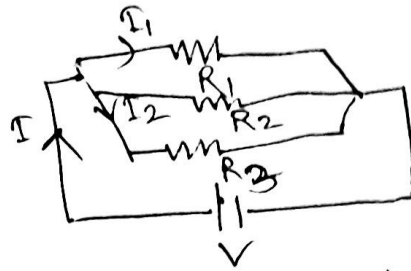

$I \rightarrow$ main current

$$I_1 = I \left\{ \frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right\}$$

$$I_2 = I \left\{ \frac{R_1 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right\}$$

$$I_3 = I \left\{ \frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right\}$$

question

(2)

Kerchhoff's ~~and~~ voltage law is concerned with

- (a) IR drop
- (b) battery ~~drop~~ emf
- (c) junction voltage.
- (d) both (a) & (b)

Ans: (c)

* What is form factor

Ans: It is defined as ratio of rms value to the avg. value of any alternating quantity.


$$K_f = \frac{\text{r.m.s. value}}{\text{avg. value}} = \frac{0.707 I_m}{0.637 I_m} = 1.1$$

*.

Power in Capacitor is

- (a) e, v , (b) $\frac{1}{2} e v$, (c) $\frac{1}{2} e v^2$, (d) $\frac{1}{2} e^2 v^2$

*

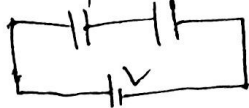

$$C_T = \frac{1}{C_1} + \frac{1}{C_2}$$

Question

- ① In a series RLC ckt. at Resonance the voltage across resistor is 10V. then the voltage across Inductor will be — time across the capacitor

Ans :- Equal time $\left(\begin{array}{l} \text{In Resonance} \\ X_L = X_C \\ I X_L = I X_C \Rightarrow V_L = V_C \end{array} \right)$

- ② If ~~1~~ 1 Amp. current flowing in a ckt the number of electrons flowing through the ckt is 1.6×10^{-19} coulombs.

- ③ The practical current source offer Ideal source Internal Resistance

- ④ In RC series ckt total voltage is 10V & voltage across Resistor is 6V then voltage across the Capacitor is

Ans :- $V_T = 10V$
 $V_R = 6V$
 $V_C = ?$

$$(V_T)^2 = (V_R)^2 + (V_C)^2$$

$$(10)^2 = (6)^2 + (V_C)^2$$

$$100 = 36 + V_C^2 \Rightarrow V_C = \sqrt{64} = 8V.$$

- ⑤ Resistances of Copper wire of $R \Omega$. This wire stretched to double length. New Resistance is $\left(\frac{R}{2} \right)$

Ans :- $R = 8 \frac{l}{A}$ — (1)
 $R = 8 \frac{2l}{A} \Rightarrow \frac{R}{2} = \frac{8l}{A}$
 $\Rightarrow \boxed{\frac{R}{2} = R_1}$

Convert rectangular to polar form

① Let $P = 3 + j4$ Convert to polar form

$$|P| = \sqrt{(3)^2 + (4)^2} = \sqrt{25} = 5$$

$$\theta = \tan^{-1}\left(\frac{y}{x}\right) = \tan^{-1}\left(\frac{4}{3}\right) = \tan^{-1}(1.33) = 53.13$$

$$\text{polar form} = 5 \angle 53.13$$

Convert polar form to Rectangular form

* Q:- $10 \angle 30$

Here magnitude 10, phase angle 30

$$\begin{aligned} \text{Real Component} &= 10 \cos 30^\circ \\ &= 10 \times 0.866 \\ &= 8.66 \end{aligned}$$

$$\begin{aligned} \text{Quadrature Component} &= 10 \sin 30^\circ \\ &= 10 \times \frac{1}{2} = 5 \end{aligned}$$

Rectangular form is

$$8.66 + j5$$

The avg. power in purely Inductive ckt
one complete cycle is

(*)

$$\textcircled{A} \quad \underline{E_{\text{rms}} I_{\text{rms}}} \quad \textcircled{B} \quad \text{Zero} \quad \textcircled{C} \quad E_{\text{max}} I_{\text{max}} \\ \textcircled{D} \quad E_{\text{max}} I_{\text{max}} / 2$$

(10) In fine (b) bilateral

Ans: Bilateral element & directional property
 (integrating in two directions)
 i.e. Variational, multi multiplier.

(11) Question
 Bilateral M/V element is like 10

Bilateral element are always directional
 equally well in two directions

Ans: High Conductivity material.

(12) Question
 in series R-L-C network the value
 $R = 10\Omega$, $L = 0.1H$ & $C = 0.01F$
 find the Q factor.

Ans: $Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{0.1}{0.01}} = \frac{1}{10} \sqrt{10} = \frac{1}{\sqrt{10}}$

Question

(1) An impedance is given by $20 \angle 30^\circ$
 find its magnitude value.

Ans: $Z = 20 \angle 30^\circ$ $R = 20 \cos 30^\circ$
 $= 20 \times \cos 30^\circ$
 $= 20 \times \frac{\sqrt{3}}{2}$
 $= 10\sqrt{3}$
 $= 17.32 \Omega$

(2)

An alternating current
 expressed as $i = 10 \sin 100\pi t$
 find avg. value & rms. value

Ans :-

$$I = 5 + 10 \sin 100\pi t$$

$$I_{av} = I_{dc} = 5 \text{ Amp.}$$

$$I_{rms} = \sqrt{5^2 + \left(\frac{10}{\sqrt{2}}\right)^2}$$

$$= \sqrt{25 + \frac{100}{2}} = \sqrt{75} = 8.66 \text{ Amp.}$$

Q1

An Impedance given by
 $20 \angle 30^\circ$ find resistance.

Ans :- $Z = 20 \angle 30^\circ$

$$R = Z \cos 30^\circ$$

$$= 20 \times \cos 30^\circ = 20 \times \frac{\sqrt{3}}{2}$$

$$= 10\sqrt{3}$$

Q:- In Inductor of resistance
 10Ω & Inductance 100mH in
parallel with 10nF capacitor find
the resonant Angular frequency
Q-factor, & B.W.

Ans :- $R = 10\Omega$

$$L = 100\text{mH} = 100 \times 10^{-3} \text{ H.}$$

$$C = 10\text{nF} = 10 \times 10^{-9} \text{ F.}$$

~~resonant~~

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$= \sqrt{\frac{1}{100 \times 10^{-3} \times 10 \times 10^{-9}}} = \frac{10^2}{(100 \times 10^{-3})^2}$$

$$= 3.16 \times 10^4 \text{ rad/s}$$

$$Q \text{ factor} = \frac{\omega_0 L}{R} = \frac{3.16 \times 10^4 \times 100 \times 10^{-3}}{10}$$

$$= 316$$

$$B.W = \frac{\omega_0}{Q} = \frac{3.16 \times 10^4}{316} = 100 \text{ rad/sec.}$$

Q:-

Difference between parallel ckt & series ckt

Series ckt	parallel ckt
① It is an acceptor ckt	① It is a rejector ckt.
② Resonant frequency $f_0 = \frac{1}{2\pi\sqrt{LC}}$	② Same.
③ At resonant frequency, the Impedance of the ckt minimum $Z = R$	③ AT Resonant frequency the Impedance Z of the ckt is max,
④ $X_L = X_C$	④ Inductive Susceptance = Capacitive Susceptance.

Question

Ex


Q. A 10Ω resistance of 15.9 mH Inductor & $159\text{ }\mu\text{F}$ capacitor are connected in parallel 200 V supply of 50 Hz . Calculate current & power factor.

Ans:- $X_L = \omega L$
 $= 2\pi fL = 2\pi \times 50 \times 15.9 \times 10^{-3}$
 $= 5\Omega$

$$I_1 = \frac{V}{R} = \frac{200}{10} = 20\text{ A.}$$

$$I_2 = \frac{V}{X_L} = \frac{200}{5} = 40\text{ A.}$$
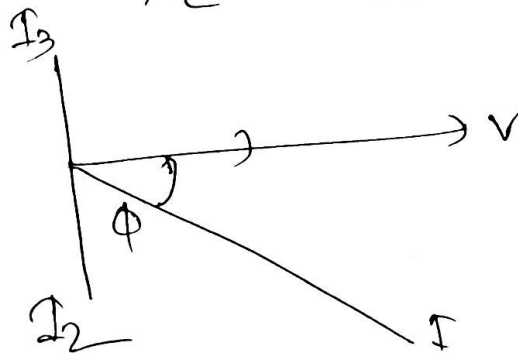
$$I_3 = \frac{V}{X_C} = \frac{200}{20} = 10\text{ A.}$$



Accordingly phasor diagram.

$$I = \sqrt{I_1^2 + (I_2 - I_3)^2}$$
$$= \sqrt{(20)^2 + (40 - 10)^2} = 36\text{ A.}$$

$$\text{P.F.} = \cos \phi = \frac{I_1}{I}$$
$$= \frac{20}{36} = 0.56 \text{ lag}$$

Q:- Under what condition ckt is said to be Resonance

Ans :- $X_L - X_C = 0$

Or $\boxed{\text{Net reactance} = 0}$

Q:- What is power factor

Ans :- ratio of Resistance to the Impedance

$$\cos \phi = \frac{R}{Z}$$


→ It has no unit.

Q:- what is the effect of low power factor

Ans :- Draw more current.

Q:- Two Impedance $Z_1 = (10 + j5)$
 $Z_2 = 8 + j6$ are connected
across the voltage $V = 200 \angle 0^\circ$

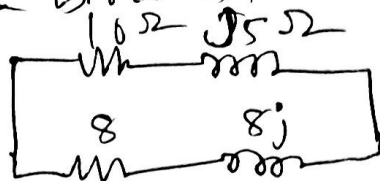Calculate ckt current; its
phase & branch current.



Soln

$$\frac{\text{Branch A}}{Y_1} = \frac{1}{Z_1} = \frac{1}{10 + j5}$$

$$Y_1 = \frac{10 - j5}{(10 + j5)(10 - j5)}$$

$$Y_1 = \frac{10 - j5}{100 + 25} = 0.08 - j0.04 \text{ Siemens}$$

Branch - B

$$\frac{1}{Z_2} = \frac{1}{8 + j6}$$

$$= \frac{8 - j6}{(8 + j6)(8 - j6)}$$

$$Y_2 = \frac{8 - j6}{64 + 36} = 0.08 - j0.06 \text{ Siemens}$$

$$Y = (0.08 - j0.04) + (0.08 - j0.06)$$

$$= 0.16 - j0.1 \text{ Siemens}$$

$$V = 200 \angle 0^\circ = 200 + j0$$

$$I = VY = (200 + j0)(0.16 - j0.1)$$

$$= 32 - j20 = 37.74 \angle -32^\circ$$

$$I_1 = VY_1 = (200 + j0)(0.08 - j0.04)$$

$$= 16 - j8 = 17.88 \angle -26.32^\circ$$

$$I_2 = VY_2 = (200 + j0)(0.08 - j0.06)$$

$$= 16 - j12 = 20 \angle -36.87^\circ$$

Q: - An alternating ~~current~~ ^{voltage}.
 $V = 200 \sin(314t)$ what will be
effective value of voltage.

Soln

$$V_m = 200$$

$$V_{\text{effective}} = V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$= \frac{200}{\sqrt{2}} = 100\sqrt{2} = 141.4 \text{ V}$$

(Q) 2. A series RLC CKT which
Resonates at $f_0 = 500 \text{ KHz}$ has.
 $L = 100 \mu\text{H}$, Resistance 25Ω &
Capacitance 1000 pF . find Quality
factor

$$\begin{aligned} \text{Ans: } Q &= \frac{1}{R} \sqrt{\frac{L}{C}} \\ &= \frac{1}{25} \sqrt{\frac{100 \times 10^{-6}}{1000 \times 10^{-12}}} \\ &= 12.6 \end{aligned}$$



STUDY MATERIAL

SUBJECT : BASIC ELECTRICAL ENGG. (BEE)

(MODULE – II)

SEMESTER : 1ST / 2ND

BRANCH : MECH/CE/EE/EEE/CSE/ETC

DEPARTMENT OF ELECTRICAL ENGINEERING
SRINIX COLLEGE OF ENGINEERING, BALASORE
(www.srinix.org)

Pracice Electrical Engg

module. 02

- ① In a 3- ϕ Balance load wattmeter.
read 2000 Watts and 500 Watts respectively
Find P.F of the ckt?

Ans:-

$$W_1 + W_2 = 2000 + 500 = 2500 \text{ W.}$$

$$W_1 - W_2 = 2000 - 500 = 1500 \text{ W.}$$

$$\tan \theta = \sqrt{3} \left\{ \frac{W_1 - W_2}{W_1 + W_2} \right\}$$
$$= 1.73 \left\{ \frac{1500}{2500} \right\}$$

$$\tan \theta = 1.0392$$

$$\theta = \tan^{-1}(1.0392) = 46.6^\circ$$

$$\cos \theta = 0.6394$$

- ② Difference between Star & Delta System -

Ans.

<u>Star Connection</u>	<u>Delta Connection</u>
------------------------	-------------------------

(1) Y Connection neutral is available

(1) neutral is not available.

(2) Power (W) = $\sqrt{3} V_L I_L \cos \theta$

(2) Power = $\sqrt{3} V_L I_L \cos \theta$.

(3) Line voltage $\sqrt{3}$ times more than phase voltage

(3) Line voltage & phase voltage is same.
 $V_L = V_P$

$$V_L = \sqrt{3} V_P$$

(4) Line current & phase current is same.

(4) Line current is $\sqrt{3}$ times more than phase current.

$$I_L = I_P$$

$$I_L = \sqrt{3} I_P$$

(5) Two types of voltage is available. i.e. between phase & neutral &

(5) only single voltage is available.

(4) What are different methods to measure 3- ϕ power.

Ans: - (1) Single wattmeter method.

(2) Two wattmeter method.

(3) 3-wattmeter method.

(5) What do you mean by Balanced & Unbalanced load.

Ans: - When the current in each phase is equal then it is a Balanced load. & if not equal it is Unbalanced load.

(6) What is the relation between line & phase current in case of Delta Connection.

Ans: - In Delta Connection, line current is equal to $\sqrt{3}$ times of phase current.

$$I_L = \sqrt{3} I_P$$

(7) How the power factor can be calculated by two wattmeter method.

$$\text{Ans: - } \cos \phi = \sqrt{3} \left\{ \frac{W_1 - W_2}{W_1 + W_2} \right\}$$

(8) Write down formula for power in star & Delta Connection.

Ans: - In Star Connection,
Power = $\sqrt{3} V_L I_L \cos \phi$.

in case of Δ Connection.

$$\text{Power} = \sqrt{3} V_L I_L \cos \theta.$$

⑨ Define phase voltage

Ans:- The voltage across single phase.
is called phase voltage.

→ It always measure between phase & neutral.

→ Symbol is (V_p)

⑩ Define phase current?

Ans:- The current flowing in any one phase is called phase current.

→ Symbol is I_p .

⑪ Define line voltage.

Ans:- The voltage across two phase.
is called line voltage.

→ It always measure between two phase.

→ It always more than phase voltage.

→ Symbol is (V_L)

⑫ Define line current?

Ans:- The current flow in each line.
Called as line current

→ in (Y) Connection.

$$I_{ph} = I_{line}$$

- (19) Three impedances each having
Resistance of 30Ω & Inductive
Reactance 15Ω are connected on $400V$,
3 ϕ supply. Calculate line current,
Power factor & power consumed?

Ans:- $Z_{ph} = 30 + j15 \Omega$.

$$V = 400V.$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231V.$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{231 \angle 0}{30 + j15} \\ = 6.80 \angle -26.56$$

In Star Connection.

$$I_{ph} = I_L = 6.80 \text{ Amp.}$$

(ii) power factor $= \cos \theta$
 $= \cos(26.56)$
 $= 0.894$

(iii) Power consumed $= \sqrt{3} V_L I_L \cos \theta$
 $= \sqrt{3} \times 400 \times 6.80 \times 0.89$
 $= 4261 \text{ watt.}$

(14) 3 equal Inductance having reactance 25Ω of reactance of 40Ω are connected in star to a $400V$, $3-\phi$, $50Hz$ system. Calculate.

(1) phase current.

(2) Line current.

(3) power factor.

(4) power consumed.
Given Data.

Ans: - $Z = 25 + j40$

$$V_L = 400V.$$

$$f = 50Hz.$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.92V.$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.92 \angle 0}{25 + j40}$$

$$I_{ph} = 0.573 \angle -86.42.$$

$$\boxed{I_{ph} = I_L}$$

(i) $I_L = 0.573 \text{ Amp.}$

(iii) power factor $\cos\theta = \cos(86.42)$
 $= 0.062$

(iv) power consumed.
 $= 3 \times V_{ph} \times I_{ph} \times \cos\theta.$
 $= 3 \times 230.92 \times 0.573 \times 0.062$

- (15) A Delta Connection. Balanced 3 ϕ load is supplied from 3- ϕ , 400V supply. If line current is 20 Amp. & power consumed by the load is 10 kW. Then find (1) ~~phase current~~ phase current.
 (2) power factor.
 (3) power consumed if the same load connection is in star.

Ans:-

$$V_L = 400V.$$

$$I_L = 20 \text{ Amp.}$$

$$\text{Power} = 10 \times 10^3 \text{ watt}$$

$$I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{20}{\sqrt{3}} = 11.54 \text{ Amp.}$$

$$P = \sqrt{3} \times V_L \times I_L \cos \phi.$$

$$10 \times 10^3 = \sqrt{3} \times 400 \times 20 \times \cos \phi.$$

$$\cos \phi = \frac{10 \times 10^3}{\sqrt{3} \times 400 \times 20}$$

$$\cos \phi = 0.721$$

$$V_{ph} = 400V$$

$$\boxed{V_L = V_{ph}}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400}{11.54} = 34.66 \Omega$$

3 ϕ load
supply.

10 kW
then.

in Y Connection

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{34.66} \\ = 6.66 \text{ Amp.}$$

4 the
on. in star.

$$\text{Power} = 3 \times 230.94 \times 6.66 \times 0.721 \\ = 3.326 \text{ kW.}$$

(16) Three Identical coils are
connected in star connection. 400V.
50 Hz, 3- ϕ supply. each coil.
Consuming 300 W. of the power.
factor 0.8 lag. Calculate.

1 Amp.

ϕ .

(1) line current.

(2) Impedance.

(3) Resistance & Inductance.

G.D
Ans:- $V_L = 400 \text{ V.}$

$$f = 50 \text{ Hz.}$$

$$\text{Power} = 300 \text{ W.}$$

$$\cos \phi = 0.8 \text{ lag.}$$

$$I_{ph} = \frac{V_L}{\sqrt{3}}$$

$$= \frac{400}{\sqrt{3}} = 230.92 \text{ Volt.}$$

26 Ω

$$(\text{Power})_{ph} = I_{ph} \times V_{ph} \times \cos \phi$$

$$= \frac{300}{230.92 \times 0.8}$$

$$I_{ph} = 1.62 \text{ Amp}$$

In Star Connection.

$$(1) \quad I_L = I_{ph}$$

$$I_L = 1.62 \text{ Amp.}$$

$$(2) \quad Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{230.92}{1.62} = 142.54$$

$$(3) \quad \cos \phi = \frac{R}{Z}$$

$$R = \cos \phi \times Z$$

$$= 142.54 \times 0.8 = 114 \Omega$$

$$\cancel{X_L} \quad \sin \phi = \frac{X_L}{Z}$$

$$X_L = Z \sin \phi$$

$$= 142.54 \times \sin(\cos^{-1} 0.8)$$

$$= 85.52 \Omega$$

$$Z_{ph} = (114 + j85.52) \Omega$$

$\cos \phi$.

7) Three identical coil each having Resistance 10Ω & Capacitance of $20\mu F$ are connected in delta to $400V$, $3-\phi$, $50Hz$ supply. Calculate line current & total power absorbed.

Ans:- Capacitive Reactance.

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi \times 50 \times 200 \times 10^{-6}}$$

$$= 15.97\Omega.$$

$$\frac{2}{3} = 1142.54$$

$$R_{ph} = 10\Omega.$$

$$Z_{ph} = \sqrt{R^2 + X_c^2} \\ = \sqrt{10^2 + 15.97^2} = 18\Omega$$

$$\text{Power factor} = \frac{R_{ph}}{Z_{ph}}$$

$$= \frac{10}{18} = 0.55.$$

$$\frac{2}{3} = 114\Omega.$$

$$\text{phase voltage} = 400V = V_{ph}.$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{18}$$

$$= 22.22A.$$

$$\frac{2}{3} (\cos 10.8)$$

2.

$$I_L = \sqrt{3} I_{ph} = \sqrt{3} \times 22.22$$

$$= 38.48A.$$

$$\text{Power absorbed} = \sqrt{3} V_L I_L \cos \phi.$$

$$= \sqrt{3} \times 400 \times 38.48 \times 0.55$$

- (18) A Balanced, 3- ϕ star connected load of 450 kW. takes a leading current of 100 A. With a line voltage 110 V, 50 Hz. Find the ckt constants of the load per phase.

$$\text{Ans :- } Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{\frac{1100}{\sqrt{3}}}{100} = 6.35 \Omega.$$

$$\text{power/phase} = I^2 R = \frac{450 \text{ kW}}{3} = 150 \text{ kW}.$$

$$(100)^2 \times R = \frac{150 \times 10^3}{3}$$

$$R = \frac{150 \times 10^3}{3 \times (100)^2} = 5 \Omega.$$

$$\begin{aligned} X &= \sqrt{Z^2 - R^2} \\ &= \sqrt{(6.35)^2 - (5)^2} \\ &= 3.9 \Omega. \end{aligned}$$

connected.

leading

line.

the ckt

phase.

$$X = X_c = \frac{1}{\omega C}$$

$$3.9 = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi \times 50 \times 3.9}$$

$$C = \frac{1}{2\pi \times 50 \times 3.9}$$

$$= 810 \text{ pF.}$$

- (19) Three similar coil each having a resistance 10Ω & Inductance of 0.04 H . are connected in star connection & delta connection. 400 V , $3-\phi$, 50 Hz . Supply. Calculate. line current, phase current, Power factor, Total power absorbed.?

Ans:- $R = 10 \Omega$
 $L = 0.04 \text{ H}.$

$$\begin{aligned} Z_{ph} &= R + jX_L \\ &= R + j\omega L \\ &= 10 + j(2\pi f)L \\ &= 10 + j12.56. \end{aligned}$$

$$Z_{ph} = \sqrt{(10)^2 + (12.56)^2}$$

$$= 16 \Omega.$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{V_L}{\frac{V_3}{\sqrt{3}} Z_{ph}}$$

$$= \frac{400}{\frac{V_3}{16}} = 14.4 A.$$

$$I_L = I_{ph} = 14.4 A.$$

$$\text{power factor } (\cos \phi) = \frac{R_{ph}}{Z_{ph}}$$

$$= \frac{10}{16} = 0.625$$

$$\text{Power} = \sqrt{3} V_L I_L \cos \phi.$$

$$= \sqrt{3} \times 400 \times 14.4 \times 0.625$$

$$= 6235.2 \text{ watt}$$

Delta

$$V_L = 400 V = V_{ph}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{16} = 25 A$$

$$\text{Line current } I_L = \sqrt{3} \times I_{ph}.$$

$$= \sqrt{3} \times 25$$

$$= 43.3 A.$$

$$\text{power Absorbed} = \sqrt{3} V_L I_L \cos \phi.$$

STUDY MATERIAL

**SUBJECT : BASIC ELECTRICAL ENGG. (BEE)
(MODULE – III)**

SEMESTER : 1ST / 2ND

BRANCH : MECH/CE/EE/EEE/CSE/ETC

**DEPARTMENT OF ELECTRICAL ENGINEERING
SRINIX COLLEGE OF ENGINEERING, BALASORE
(www.srinix.org)**

What is Residual magnetism?

Ans:- The magnetism remain in the magnetic material after removing the magnetizing force is called Residual Magnetism.

→ When current is passed through a coil wound on a soft iron, it will become magnet & when current is reduced to zero, there is still some magnetism left in the soft iron piece that is called residual magnetism.

→ Define Magnetic flux density?

Ans:- Magnetic flux ϕ per unit area is called Magnetic flux density.

→ It is denoted as B

$$\rightarrow B = \frac{\text{Magnetic flux}}{\text{Area}} = \frac{\phi}{A}$$

→ Unit is Wb/m^2

→ Define MMF?

Ans:- It is a force which drives the magnetic lines of force in a magnetic field.

→ Unit is Ampere 'turns'.


Q:- Find the Reluctance of a magnetic field having Core length 50 cm & crosssectional area 10 cm^2 . Assume relative permeability 1500 for the core.

Soln

$$\begin{aligned} \text{Reluctance} = (R) &= \frac{1}{\mu A} = \frac{1}{\mu_0 \mu_r A} \\ &= \frac{1}{4\pi \times 10^{-7} \times 1500 \times 10 \times 10^{-4}} = 2.65 \times 10^5 \text{ AT/Wb} \end{aligned}$$

3)

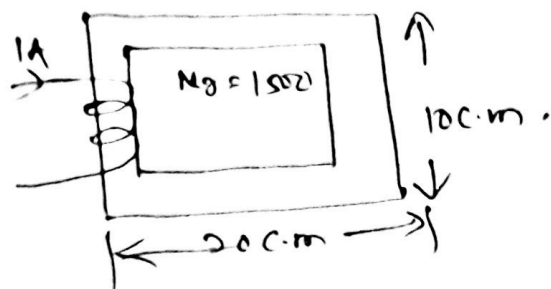Example :- find the net magnetic flux in the core for simple magnetic ckt shown in fig. Assume that the core has Uniform cross section throughout equal to 1 cm^2 . The coil has 200 turns.



$$L = 20 + 10 + 20 + 10 = 60 \text{ cm} = 0.6 \text{ m.}$$

$$A = 1 \text{ cm}^2 = 10^{-4} \text{ m}^2$$

$$\mu = \mu_0 \mu_r = (4\pi \times 10^{-7}) \times 1500 = 6\pi \times 10^{-4} \text{ H/m}$$

$$R = \frac{1}{\mu A} = \frac{0.6}{6\pi \times 10^{-4} \times 10^{-4}} = 3.18 \times 10^6 \text{ AT/Wb.}$$

$$\text{mmf} = NI = 200 \text{ AT}$$

$$\phi = \frac{\text{mmf}}{R} = \frac{200}{3.18 \times 10^6} = 62.9 \times 10^{-6} \text{ Wb}$$

EX :- A coil is wound uniformly with 300 turns over a steel ring of relative permeability 900 having a mean circumference 40 cm. & cross-sectional Area of 5 cm^2 . If the coil has resistance 100Ω & is connected to 230V dc supply. Calculate (i) mmf (ii) field strength (iii) Reluctance of ring (iv) permeance.

current carrying by a coil (I) = $\frac{V}{R} = \frac{250}{100} = 2.5 \text{ A}$

(i) mmf of coil = $NI = 300 \times 2.5 = 750 \text{ AT}$.

(ii) field strength (H) = $\frac{NI}{l} = \frac{750}{0.4} = 1875 \text{ AT/m}$.

(iii) flux density $B = \mu_0 \mu_r H$
 $= 4\pi \times 10^{-7} \times 900 \times 1875$
 $= 2.12 \text{ Wb/m}^2$

Total flux (Φ) = $B \times a = 2.12 \times 5 \times 10^{-4}$
 $= 10.6 \times 10^{-4} \text{ Wb}$

(iv) Reluctance = $S = \frac{\text{mmf}}{\text{flux}}$
 $= \frac{750}{10.6 \times 10^{-4}} \text{ AT/Wb}$

(v) permeance = $\frac{1}{S} = \frac{1}{70.75 \times 10^4}$
 $= 1.4 \times 10^{-6} \text{ Wb/AT}$

Q:- find the Number of turns required to produce a flux density of 2π on the core of mean magnetic length of 260cm when the coil carries a current of 5A . Assume the permeability of the core is 1000 .

Sol:- $N = ?$ $B = 2 \text{ tesla}$ $l = 260\text{cm}$
 $I = 5\text{A}$ $\mu_r = 1000$

We know that field strength $H = \frac{B}{\mu}$
 $H = \frac{B}{\mu_0 \mu_r} = \frac{B}{4\pi \times 10^{-7} \times 1000}$
 $= \frac{2 \times 10^{-3} \times 10^{-3}}{4\pi}$
 $= \frac{1}{2\pi} \times 10^{-4} \frac{\text{AT}}{\text{m}}$

1)

but

$$H = \frac{NI}{l}$$

$$\frac{1}{2\pi} \times 10^4 = \frac{N \times 5}{30 \times 10^{-2}}$$

$$\Rightarrow N = \frac{10^4 \times 20 \times 10^{-2}}{2\pi \times 5} = 64$$

Q:- Define Relative permeability?

Ans:- The ratio of the absolute permeability of magnetic material to the absolute permeability of non-magnetic material is called Relative permeability?

→ it is denoted as μ_r

$$\rightarrow \boxed{\mu_r = \frac{\mu}{\mu_0}}$$

Q:- An Iron ring has mean circumference length 20cm & cross sectional of 1cm^2 . It is wound with 100 turns. Uniformly & carries a current of 0.05A. The flux is 3mweber. find (a) flux density (b) field intensity (c) permeability (d) Relative permeability. (e) Reluctance.

Solⁿ :-

$$L = 20\text{cm} = 0.2\text{m}.$$

$$A = 1\text{cm}^2 = 1 \times 10^{-4}\text{m}^2$$

$$I = 0.05\text{Amp}.$$

$$\text{flux } \phi = 3\text{mweber} = 3 \times 10^{-6}\text{weber}.$$

$$N = 100\text{turns}.$$

Soln

$$\text{Flux density } B = \frac{\text{flux}}{\text{Area of cross section}} \\ = \frac{3 \times 10}{1 \times 10^{-4}} = 0.03 \text{ wb/m}^2$$

$$\text{Field Intensity } H = \frac{NI}{l} = \frac{100 \times 0.05}{0.2} = 25 \text{ AT/m.} \\ \text{permeability } (\mu) = \frac{B}{H} \\ = \frac{0.03}{25} = 1.2 \times 10^{-3} \text{ henry/m}$$

Relative permeability

$$\mu_r = \frac{\mu}{\mu_0} = \frac{1.2 \times 10^{-3}}{4\pi \times 10^{-7}} = 954.92.$$

Reluctance

$$= \frac{25}{3 \times 10^{-6}} = 8.33 \times 10^6 \text{ AT/web.}$$

Q Determine the flux density at a point 60 mm in air from a long straight conductor carrying a current of 500 A.

Soln

$$d = 60 \text{ mm} = 60 \times 10^{-3} \text{ m}$$

$$I = 500 \text{ A.}$$

$$H = \frac{I}{2\pi d} = \frac{500}{2\pi \times 60 \times 10^{-3}}$$

$$B = \mu_0 H = 4\pi \times 10^{-7} \times \frac{500}{2\pi \times 60 \times 10^{-3}} \\ = 1.67 \times 10^{-3} \text{ T}$$

Q: A coil of Insulated wire of 500 turns & of Resistance 4Ω is closely wound on an Iron ring. The ring has a mean diameter of 0.25m & Uniform crosssectional area of 700mm^2 . Calculate total flux in the ring when a d.c supply of 6V. is applied to the end of the winding. Assume a relative permeability of 550.

Soln

$$I = \frac{V}{R} = \frac{6}{4} = 1.5\text{A.}$$

$$N = 500, \quad l = \pi d = \pi \times 0.25\text{m.}$$

$$a = 700\text{mm}^2 = 700 \times (10^{-3})^2 = 700 \times 10^{-6}\text{m}^2 \\ = 7 \times 10^{-4}\text{m}^2$$

$$H = \frac{IN}{l} = \frac{1.5 \times 500}{\pi \times 0.25} = 955\text{A/m.}$$

$$B = \mu_0 \mu_r H = 4\pi \times 10^{-7} \times 550 \times 955 \\ = 0.66\text{AT}$$

$$\Phi = Ba = 0.66 \times 7 \times 10^{-4} \\ = 0.462\text{mwb.}$$

Q:- Define ohm's law in Magnetic ckt & Electric ckt.

Ans:- magnetic ckt = $\frac{\text{mmf}}{\text{Reluctance}}$

$$\text{Current} = \frac{\text{mmf}}{\text{Resistance}}$$

The Electric ckt -

- Q:- A mild steel ring having cross-sectional area of 500 mm^2 & mean circumference of 400 mm has coil of 200 turns wound uniformly over it. Calculate (a) Reluctance of the ring (b) current to produce 80 mWb in the ring. Assume relative permeability of the material 1000.

Soln Reluctance $S = \frac{1}{\mu_0 \mu_r N^2 A}$

$$= \frac{1}{4\pi \times 10^{-7} \times 1000 \times 500 \times 10^{-6} \text{ m}^2}$$

$$= 63.6 \times 10^4 \text{ AT/Wb.}$$

$$\text{Current}(NI) = \frac{\text{mmf}}{\phi S} = \phi S$$

$$\Rightarrow NI = \text{mmf} = \phi S$$

$$\Rightarrow NI = \phi S$$

$$I = \frac{\phi S}{N} = \frac{80 \times 10^{-6} \times 63.6 \times 10^4}{200}$$

$$= 2.54 \text{ A.}$$

Q:- what are factor on which the reluctance depends.

Ans:- (1) Directly proportional to the length of flux path.

(2) inversely proportional to cross-sectional Area.

$$(3) S = \left(\frac{1}{\mu_0 \mu_r N^2 A} \right) \text{ AT/Wb.}$$

* what are the classes of magnet

Ans:- magnets are classified into two classes

(a) permanent magnet

(b) Electro-magnet.

Q:- Application of Biot-Savart law

- (1) magnetic field strength due to a finite length of wire.
- (2) magnetic field strength along the axis of a square coil.
- (3) magnetic force on the axis of circular coil.

Q:- Define Ampere turn

Ans:- $\rightarrow$ It is the Unit of mmf

$\rightarrow$ It is given by the product of number of turn of magnetic ckt and the current in ampere in these turns.

$$AT = H \times L$$

Q - Difference between Electric ckt & magnetic ckt.

① flux = $\frac{\text{mmf}}{\text{Reluctance}}$

$\rightarrow$ mmf is AT

$\rightarrow$ flux density (wb/m^2)

$\rightarrow$ Reluctance
 $= \frac{1}{\mu A}$

$\rightarrow$ permeability
 $= \frac{1}{\text{Reluctivity}}$

$\rightarrow$ current = $\frac{\text{emf}}{\text{resistance}}$

$\rightarrow$ emf is volt.

$\rightarrow$ current density (A/m^2)

$\rightarrow$ Resistance
 $R = \rho \frac{L}{A}$

$\rightarrow$ Conductivity
 $= \frac{1}{\text{Resistivity}}$

STUDY MATERIAL

**SUBJECT : BASIC ELECTRICAL ENGINEERING (BEE)
(MODULE – IV)**

**SEMESTER : 1ST / 2ND
[ALL BRANCHES]**

CONTENTS :

- **SHORT TYPE QUESTIONS AND ANSWERS**
- **LONG TYPE QUESTIONS AND ANSWERS**

**DEPARTMENT OF ELECTRICAL ENGINEERING
SRINIX COLLEGE OF ENGINEERING, BALASORE
(www.srinix.org)**

Q1:- A 10 KVA - ϕ - Transformer has core area of $200/23$. The primary is connected to 1500V, 60 Hz supply. Find the secondary voltage on open ckt & approximate value of the current of two winding on full load. Find the max. value of the flux.

Ans:- we know that

$$\begin{aligned} \text{E/P Voltage} &= 10 \text{ KVA} \\ &= 10 \times 10^3 \text{ V} \end{aligned}$$

$$E_2 = \frac{N_2}{N_1} \times E_1$$

$$= \frac{23}{200} \times 1500 = 115 \text{ volt.}$$

$$I_1 = \frac{\text{E/P KVA}}{V_1} = \frac{10,000}{1500} = 6.67 \text{ A.}$$

$$I_2 = \frac{V_1}{V_2} \times I_1 \Rightarrow \frac{10000}{1500} \times 6.67 = 87 \text{ A.}$$

$$\text{max flux } \phi_m = \frac{E_1}{4.44 f N_1}$$

$$= \frac{1500}{4.44 \times 60 \times 200}$$

$$= 18.75 \text{ mwb.}$$

Q:- The maximum flux density in the core 250/3000 volt, 50 Hz single phase transformer 1.2 wb/m^2 . If the emf per turn is 8 volt. determine primary & secondary turns area of the core.

Soln

$$E_1 = 250,$$

$$E_1 = N_1 \times \text{emf induced/turn.}$$

$$N_1 = \frac{250}{8} = 32$$

$$N_2 = \frac{3000}{8} = 271$$

$$(11) \quad E_2 = 4.44 f N_2 B_m X A$$

$$3300 = 4.44 \times 50 \times 375 \times 1.2 \times A$$

$$\boxed{A = 0.003 \text{ m}^2}$$

Q:- Calculate emf in the two winding of 1- ϕ fully loaded Transformer of 1000/200V, 25 KVA rating, neglect no load current in Transformer.

Soln

Given:

$$V_1 = 1000 \text{ V}, \quad V_2 = 200 \text{ V}$$

$$V_1 I_1 = 25 \text{ KVA} \\ = 25000 \text{ VA}$$

$$I_1 = \frac{V_1 I_1}{V_1} = \frac{25000}{1000} = 25 \text{ A}$$

$$I_2 = \frac{V_2 I_2}{V_2} = \frac{25000}{200} = 125 \text{ A}$$

Q:- The primary winding of a 1- ϕ Transformer is connected to a 220V, 50 Hz supply. The secondary winding has 2000 turns. If the max. value of the core flux 0.003 Wb, Determine (a) no of turns in the primary winding (b) induced emf in secondary winding.

Soln

$$\therefore V_1 = 220 \text{ V}, \quad f = 50 \text{ Hz}, \quad \phi_m = 0.003 \text{ Wb} \\ N_2 = 2000$$

$$E_1 = 4.44 f \phi_m N_1$$

$$\Rightarrow N_1 = \frac{220}{4.44 \times 50 \times 0.003} = 330 \text{ turns}$$

Since $\frac{E_2}{E_1} = \frac{N_2}{N_1}$

$$E_2 = \left(\frac{N_2}{N_1} \right) E_1$$

$$= \left(\frac{2000}{330} \right) \times 220 = 1333 \text{ V.}$$

Ex:- The eddy current loss in an iron core is 1 kW. when excited 200V, 50 Hz supply what will be the loss when supply frequency changed 25 Hz

Solⁿ

$$\left(\frac{W_e}{W_e'} \right) = \left(\frac{f}{f'} \right)^2 \quad \underline{\text{G.D}}$$

$$\Rightarrow \left(\frac{W_e}{W_e'} \right) = \left(\frac{50}{25} \right)^2 \quad W_e = 1 \text{ kW}$$

$$\Rightarrow \left(\frac{W_e'}{W_e} \right) = \left(\frac{1}{2} \right)^2 \quad W_e = 1 \times 10^3 \text{ W}$$

$$\Rightarrow \frac{W_e'}{W_e} = \frac{1}{4}$$

$$\Rightarrow W_e' = \frac{1 \times 10^3}{4} = \frac{1000}{4} = 250 \text{ Watts}$$

Ex:- A 3300/230, 50 Hz, 1- ϕ -Transformer is to be worked at maximum flux density of 1.2 T in core. The effective cross-sectional area of a core 150 m². Calculate suitable value primary & secondary turns. $E_1 = 3300$

Ans:-

$$E_1 = 4.44 B_m A f N_1$$

$$N_1 = \frac{E_1}{4.44 \times B_m \times A \times f}$$

$$= \frac{3300}{4.44 \times 1.2 \times 150 \times 50}$$

$$= 826 \text{ turns}.$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} \Rightarrow N_2 = \frac{230}{3300} \times 826$$

$$= 58 \text{ turn}.$$

Q:-3 Define slip

Ans:- The difference between synchronous speed & rotor speed is called slip.

→ It is denoted as 's'

$$\% \text{ slip} = \frac{\text{Synchronous speed} - \text{Rotor speed}}{\text{Synchronous speed}} \times 100$$

$$\boxed{\% s = \frac{N_s - N_r}{N_s} \times 100}$$

Ex A 8 pole alternator runs at 750 rpm. & supplies power to 6 pole Induction motor. which has full load slip 3%. Find the full load speed of the Induction motor.

Solⁿ Number of poles of alternator = 8
Speed = 750 rpm.

$$f = \frac{P \times N}{120} = \frac{8 \times 750}{120} = 50 \text{ cycle/sec.}$$

Supply frequency = 50 cycle/sec

Now the slip $= 3\% = 0.03$

$$N_s = \frac{120 \times f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm.}$$

$$\begin{aligned} \text{Motor speed} &= N_o = N_s(1-s) \\ &= 1000(1-0.03) \\ &= 970 \text{ rpm.} \end{aligned}$$

Q:- A 100 KVA, 6600/440V, 50 Hz, 1- ϕ Transformer
80 turns on low voltage winding calculate.

(a) max. flux in a core.

(b) The number of turns on the high-voltage winding

(c) The current in each winding

Solⁿ

$$E_2 = 4.44 \phi_m f N_2$$

$$\phi_m = \frac{440}{4.44 \times 50 \times 80} = 24.8 \text{ mWb.}$$

$$\text{or } \frac{440}{6600} = \frac{80}{N_1}$$

$$N_1 = 1200 \text{ turns.}$$

$$I_1 = \frac{100 \text{ KVA}}{6600} = \frac{1000}{66} = 15.15 \text{ A.}$$

(1V)

$$\begin{aligned} \frac{I_1}{I_2} &= \frac{V_2}{V_1} \Rightarrow I_2 = I_1 \times \frac{V_1}{V_2} \\ &= 15.15 \times \frac{6600}{440} = 227.25 \end{aligned}$$

* Difference between practical Transformer and Ideal Transformer

Ans

practical T/F

① winding Resistance present

Ideal Transformer

① winding resistance neglected.