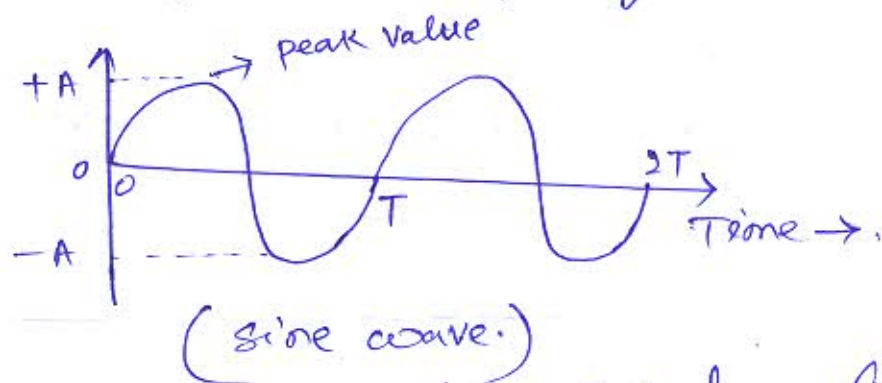


Representation of sine functions as Rotating phasor.

- The phase of an alternating quantity at any instant in time can be represented by a phasor diagram, so phasor diagrams can be thought of as "functions of time".
- A complete sine wave can be constructed by a single vector rotating at an angular velocity of $\omega = 2\pi f$, where 'f' is the frequency of the waveform.



- A generalized sinusoid is defined as follows


$$x(t) = A \sin \omega t = A \sin 2\pi ft.$$

where A is amplitude, ω is radian frequency

f = natural frequency.

$$\omega = 2\pi f \text{ (radian/sec).}$$

Phasor Diagrams ∴ →

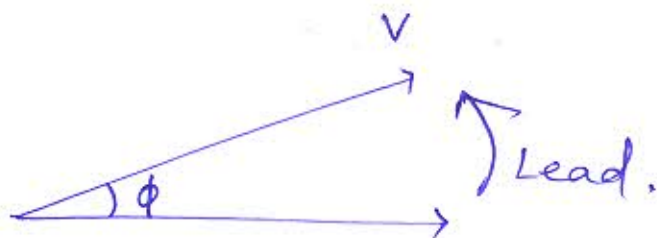

- phasor diagrams are a graphical way of representing the magnitude and directional relationship between two or more alternating quantities.

(2)

→ sinusoidal waveforms of the same frequency can have a phase difference between themselves which represents the angular difference of the two sinusoidal waveforms.

Impedance and Admittance. ∴ →

→ Admittance is defined as, where Y is the admittance, measured in siemens, Z is the impedance, measured in ohms.

→ Resistance is a measure of the opposition of a circuit to the flow of a steady current, while impedance takes into account not only the resistance but also dynamic effects.
(Known as Reactance)

$$Y = \frac{1}{Z}$$

In R-L Series circuit.

$$Z = \sqrt{R^2 + X_L^2}$$

$$X_L = \omega L = 2\pi fL$$

In R-C Series circuit.

$$Z = \sqrt{R^2 + X_C^2}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$

In R-L-C Series circuit.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

AC Circuit Analysis.

(3)

→ An a.c. circuit is one in which the magnitude of the current changes periodically with time.

→ The a.c. is produced by an alternating voltage supply.

→ The pattern of the a.c. voltage is sinusoidal in nature, that is it varies like the sine curve with constant amplitude and frequency.

→ Average value = $\frac{\text{Area under the curve.}}{\text{length of the base of the curve.}}$

→ RMS value = $\sqrt{\frac{\text{Area of half cycle wave squared.}}{\text{Half cycle base.}}}$

→ Form factor :→ The ratio of rms value to average value of an alternating quantity is known as form factor. It is represented by K_f .

$$K_f = \frac{\text{R.M.S. value.}}{\text{Average value.}}$$

→ Peak factor :→ The ratio of maximum value to the rms value of an alternating quantity is known as peak factor or amplitude factor. It is represented by K_a .

$$K_a = \frac{\text{Maximum value}}{\text{R.M.S. value.}}$$

FUNDAMENTALS OF POWER (4)

Power

- * The ability of work done is known as power.
- * The rate of consumption of energy is known as power.

Power In DC Ckt :-

- Power is product of voltage & current.

$$P = VI$$

Power In AC Ckt :-

- The rate of change of energy w.r.t time in terms of voltage & current.
- In an AC ckt the voltage & current are continuously changing. Hence power value changes w.r.t time.
- The average value of varying power is

$$P_{av} = \frac{1}{T} \int_0^T p \cdot dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} p \cdot dt$$

- The average power is also called as active power or true power.

Euler Identity :-

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$I = 5e^{j0} = 5 \angle 0 = 5 + j0$$

Power System:-

- > Generation, transmission & distribution, system are the main component of an electrical power system.
- > Generating station & distribution system are connected through a transmission line.
- > Electric power system is the combination of components that transforms other types of energy into electrical energy and transmits this energy to the consumer.

POLAR FORM

-> $A \angle \theta$

EX $10 \angle 30$

-> Multiplication & Division.

Addition

* $(2+j3) + (4+j5)$
 $= 6+j8$

* $(2+j3) + 3 \angle 30$
 $= 2+j3 + 2.59 + j1.5$
 $= 4.59 + j4.5$

Division

* $\frac{10 \angle 30}{2 \angle 50}$
 $= 5 \angle 30 - 50$
 $= 5 \angle -20$

* $(6+j8) \div 10 \angle 5$
 $= (10 \angle 53.13) \div (10 \angle 5)$
 $= 1 \angle 53.13 - 5$

RECTANGULAR FORM

-> $Z = R + jX$

EX $2 + j5$

-> Addition & subtraction.

Multiplication

$2 \angle 30 \times 5 \angle 40$
 $= 10 \angle 30 + 40$
 $= 10 \angle 70$
* $(3-j6) \times 5 \angle 10$
 $= (6.70 \angle -63.43) \times 5 \angle 10$
 $= 33.5 \angle (-63.43 + 10)$
 $= 33.5 \angle -53.43$

PROB
Two
are
the
recta
solv

$\frac{Z_1}{Z_2}$
 $= \frac{(2+j3)}{(2+j5)}$
 $= \frac{(2+j3)(2-j5)}{(2+j5)(2-j5)}$
 $= \frac{4-j10+j6-15}{4-25}$
 $= \frac{-11-j4}{-21}$
 $= \frac{11+j4}{21}$
 $= 0.52 \angle 20.1$

PROBLEM

Two impedances $Z_A = (25 - j16)$, $Z_B = (3 + j9)$ are connected in parallel in a ckt. Calculate the equivalent impedance for the given ckt in rectangular form.

Sol $Z_A = 25 - j16$

$$Z_B = 3 + j9$$

$$Z_{eq} = \frac{Z_A Z_B}{Z_A + Z_B}$$

$$= \frac{(25 - j16)(3 + j9)}{(25 - j16) + (3 + j9)}$$

$$= \frac{(29.68 \angle -32.61)(9.48 \angle 71.5)}{28 - j7}$$

$$= \frac{281.366 \angle -38.89}{28 - j7}$$

$$= \frac{281.366 \angle -38.89}{28.86 \angle -14.03}$$

$$= 9.74 \angle 52.9$$

$$= 5.875 + j7.76 \text{ (Ans)}$$

TYPES of POWER

1. Active power / True power / Real power
2. Reactive / Pulsating power
3. Apparent power = $|V| |I|$
4. Complex power = $V I^*$
(I^* = complex conjugate of I)

⑦ 1. INSTANTANEOUS & AVERAGE POWER

→ In an AC ckt the power at any instant is called SO.

→ It is equal to the product of the values of voltage & current at any instant.

→ In an ac ckt let the instantaneous value of the voltage & current.

$$V = V_m \sin \omega t$$

$$I = I_m \sin (\omega t - \phi)$$

Where, ϕ = phase angle betⁿ V & I.

→ Instantaneous power $P = VI$.

$$= V_m \sin \omega t \times I_m \sin (\omega t - \phi)$$

$$= V_m I_m \sin \omega t \cdot \sin (\omega t - \phi)$$

$$= \frac{1}{2} V_m I_m [\cos \phi - \cos (2\omega t - \phi)]$$

$$\left[\because \cos A \cdot \cos B = \frac{1}{2} [\sin (A+B) + \sin (A-B)] \right]$$

$$= \frac{1}{2} V_m I_m \cos \phi - \frac{1}{2} V_m I_m \cos (2\omega t - \phi)$$

→ The second term of right hand side of the above eqⁿ contains a double frequency 2ω . So the magnitude of the average value of the 2nd term is zero. It is because average of a sinusoidal quantity of double frequency over a complete cycle is zero. Hence the 2nd term is avoided..

$$P_{av} = \frac{1}{2} V_m I_m \cos \phi$$

→ The instantaneous power is the average power in AC ckt.

$$\begin{aligned} P_{av} &= \frac{1}{2} V_m I_m \cos \phi \\ &= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi \end{aligned}$$

Whe

F
2. F
→ R
ele
→ T
curr
is

→ F

→ f

3.

→ -

&

→ 2

→ -

(

$$P_{AV} = VI \cos \phi$$

Where, $V = \frac{V_m}{\sqrt{2}}$ = rms value of the voltage in AC ckt. (8)

$I = \frac{I_m}{\sqrt{2}}$ = rms value of current in AC ckt.

$$P = VI \cos \phi$$

P = Active power.

Reactive power :- (VAR)

→ Reactive power generates from reactive element (inductance & capacitance).

→ The product of RMS value of voltage & current with the sine of the angle between them is called the reactive power in AC ckt.

$$Q = VI \sin \phi$$

→ Reactive power for purely inductive ckt.

$$Q_L = V_L I = I^2 X_L = \frac{V_L^2}{X_L}$$

Where, X_L = Inductive reactance.

$$X_L = \omega L = 2\pi fL$$

→ Reactive power for purely capacitive ckt.

$$Q_C = V_C I = I^2 X_C = \frac{V_C^2}{X_C}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$

3. Complex power :-

→ The product of RMS value of the voltage & current in a ckt is called complex power.

→ It is represented by 'S' & its unit is VA.

→ In complex form

$$S = P + jQ \quad \text{or} \quad S = P - jQ$$

(for inductive ckt) (for capacitive ckt)

- Magnitude of the Complex power of $S = \sqrt{P^2 + Q^2}$
- If the voltage across & the current in a certain load is expressed as

$$S = VI^*$$

$$V = |V| \angle \alpha$$

$$I = |I| \angle \beta$$

$$I^* = |I| \angle -\beta$$

$$= |V| \angle \alpha \cdot |I| \angle -\beta$$

$$= |V| |I| \angle (\alpha - \beta)$$

(In polar form)

- In Rectangular form, Complex power $S = |V| |I| \cos(\alpha - \beta) - j |V| |I| \sin(\alpha - \beta)$
(For capacitive CK+)
- $S = |V| |I| \cos(\alpha - \beta) + j |V| |I| \sin(\alpha - \beta)$
(For inductive CK+)

- Reactive power Q will be +ve when the angle betⁿ V & I will be +ve ($\alpha > \beta$), which means the current is lagging to the voltage
- similarly Reactive power Q will be +ve for ($\beta > \alpha$). which indicates that current is leading to the voltage.

POWER TRIANGLE :-

- It is the geometrical representation of the apparent power, Active power & reactive power.
- In an Inductive load the impedance triangle by (Z^2) , we get the power triangle which is shown in fig-2. are shown in fig.
- Multiplying each side of the impedance triangle by (I^2) , we get the power triangle which is shown in fig-2.

Po
 → P
 → P
 → P
 → P
 eq
 bet
 cur
 → F
 also
 to
 → P
 → F

