

# CH-4-INVERTER

INVERTER: Inverter is a device which converts D.C power to A.C power at certain o/p voltage & frequency or at a certain current level & frequency.

## Application of Inverter

- (1) variable speed A.C motor drives.
- (2) Adjustable a.c drives.
- (3) Induction heating
- (4) Uninterruptible power supplies.
- (5) HVDC transmission line ( $\pm 2000$  MW)

↳ It is well known fact that Rectifier is a device which produces d.c output from an a.c source.

↳ But so many applications need of variable a.c voltage from a fixed d.c supply.

↳ The Inverters that are discussed in this chapter are so designed to meet the requirement of a.c o/p from a d.c source & can be defined as a device, which produces variable or fixed a.c voltage from a fixed or variable d.c source.

## CLASSIFICATION OF INVERTER

Inverters are classified according to type of input applied as

- (i) voltage source inverter <sup>(VSI)</sup> OR voltage driven inverter OR voltage fed inverter.
- (ii) current source inverter <sup>(CSI)</sup> OR current driven inverter OR current fed inverter.
- (iii) variable D.C linked inverter.

(i) VSI → It is the one in which d.c source has small or negligible impedance

or  
In other word it has stiff d.c voltage source at its input terminals.

Simply if i/p voltage of an inverter is maintained constant is called VSI or voltage fed inverter.

(ii) CSI → CSI is the one in which d.c source has high or infinite impedance.  
In other word it has stiff d.c source at its i/p terminals which are variable



Simply if  $i_p$  current of an inverter is maintained constant is called current fed inverter.

Variable-DC Linked Inverter

If the  $i_p$  voltage of an inverter is controllable it is called as variable-DC linked inverter.


Inverters are also classified as follows depending upon the connection of commutating component with the main ckt

- (a) Series Inverters
- (b) Parallel Inverters.
- (c) Bridge Inverters.
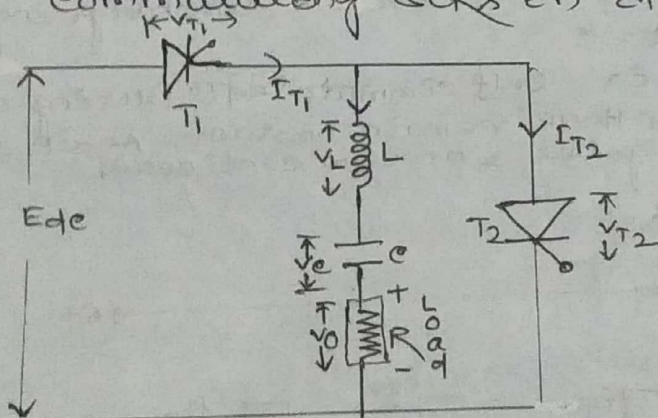
### VOLTAGE SOURCE SERIES INVERTER

↳ Inverters in which commutating elements are connected in series with the load are called Series Inverter.

↳ These inverters uses class A type commutating SCR in its ckt.



In the ckt  $E_{dc}$  is the d.c supply,  $T_1$  is the main SCR,  $T_2$  is supporting SCR,  $L$  &  $C$  are commutating elements, where  $V_O$  is the Load voltage,  $V_C$  is the voltage across the capacitor.

-  $V_L$  → voltage across the Inductor.

$I_{T1}, I_{T2}$  → current flowing through SCR-1, SCR-2

$I_O$  → Load current.

### OPERATION

The operation of Series inverter is explained with the help of wave form.

At  $t = 0$ ,

$T_1$  is gated but  $T_2$  is not gated

$T_1$  turns ON

$T_2$  is OFF



As the nature of ckt is underdamped  $i_o$  reached its peak value & then falls to zero, say at  $a$ , up to this point capacitor starts charging.

AT  $t=a$ .

$T_1$  is OFF due reverse direction of  $I_o$  till  $t=b$ ,  $T_2$  is also OFF, Hence  $i_o=0$  there fore the period  $ab$  is called Turn-off period ( $T_{off}$ )  $T_1$  &  $T_2$  are OFF the Load terminals are open ckted, Capacitor charging voltage remains constant. & Voltage across Inductor  $(V_L) = -L di/dt$ .

AT  $t=b$


$T_2$  is gated &  $T_1$  is OFF.

A Loop is formed through  $T_2$ , R-Load, c&L  $i_o = -I_o$

Now capacitor starts discharging.

AT  $t=c$

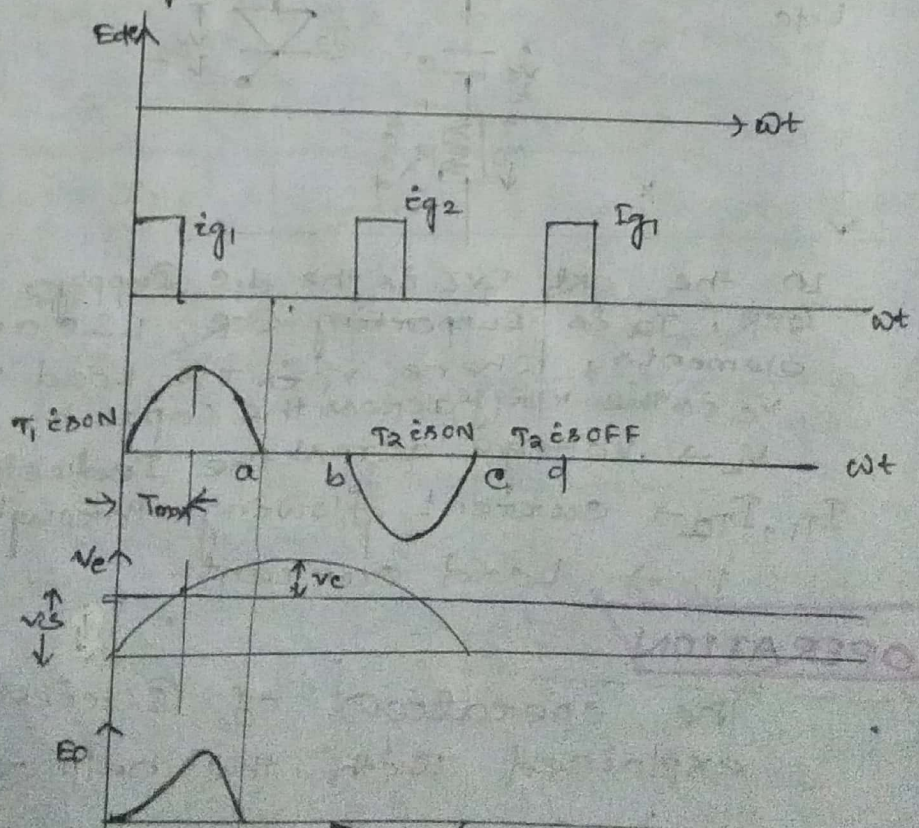
$i_o=0$ ,  $T_2$  is self commutation. During cd capacitor voltage remain constant. Again at  $t=d$ ,  $T_1$  is gated & process continues.




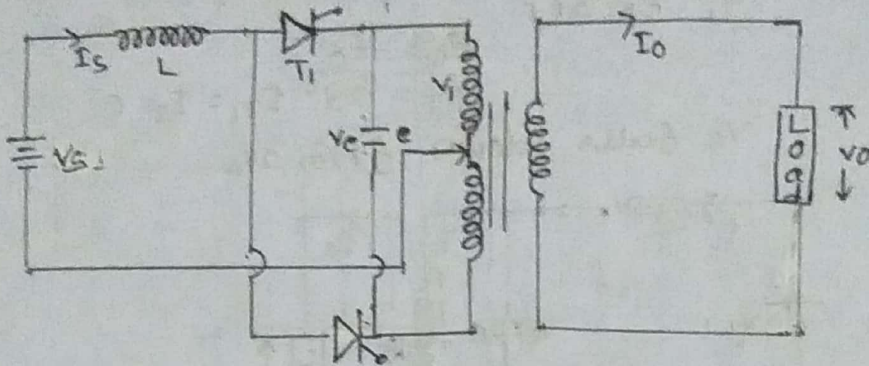
# VOLTAGE SOURCE PARALLEL INVERTER

This ckt consist of two Core  $T_1$  &  $T_2$ , Commutating capacitor  $C$ , Inductor  $L$  & output T/F with turns ratio  $N_1 : N_2$



In the ckt diagram  
 $V_s$  → Supply voltage or source voltage.  
 $V_o$  → Load voltage.  
 $V_c$  → voltage across commutating capacitor.  
 $V_1$  → Voltage across primary half of the T/F  
 $I_{T1}, I_{T2}$  → current across  $C_{OR1}$  &  $C_{OR2}$ .  
 $I_s$  → source current.  
 $I_e$  → discharging current.

## OPERATION

The operation of basic parallel inverter is explained with help of four modes.

Mode-01 at  $t=0$ ,

↳ Source current ( $I_s$ ) starts flowing through primary winding which according to Faraday's Law of Electromagnetic Induction the volt induced emf  $V_1$  ( $\approx V_s$ ) across first half of the primary winding (same is the case across second half also (according potential division rule))

↳ Therefore total induced voltage across primary winding equal to the sum of voltages across two halves of primary winding which is equal to twice the supply voltage. Now voltage across capacitor


$$V_c = 2V_1 \approx 2V_s$$

$T_1$  is ON as it is gated &  $T_2$  is OFF.

$$I_{T1} = I_s = I_o$$

$$V_c = 2V_1 = 2V_s \approx V_c$$

$$V_o = V_s$$

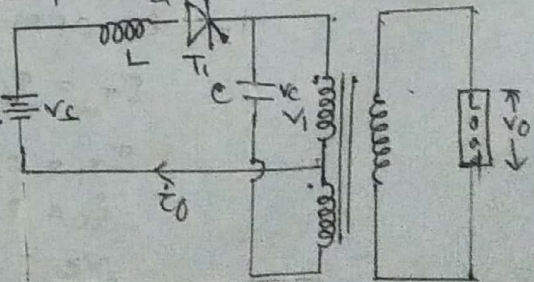

Mode-02 at  $t=0$

↳ From this instant capacitor starts discharging its stores  $2V_s$  amount of voltage across  $C_{OR1}$  there by Reverse biasing it.



$\hookrightarrow$  Hence  $T_1$  is turned off. Also at the same time this capacitor discharging voltage appear across first half of the primary establishing discharge current in negative direction to flow across capacitor charges  $+2V_s$  at  $t=t_1$


$T_2$  is ON as it gated  $\dot{e}t$ .

$T_1$  is OFF.

$$\dot{e}_c = -\dot{e}_0$$


$$\dot{e}_T = 0, I_{T1} = I_s = 0$$

$V_c$  falls down from  $2V_s$

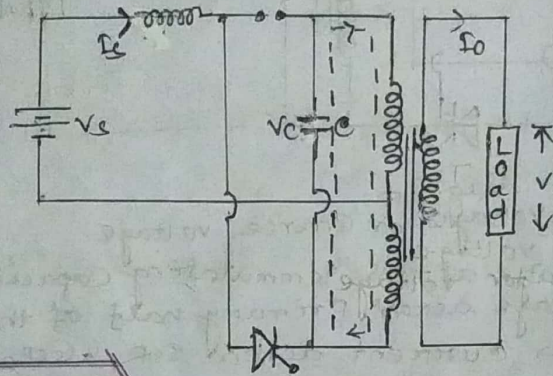

Mode-03

OPERATION

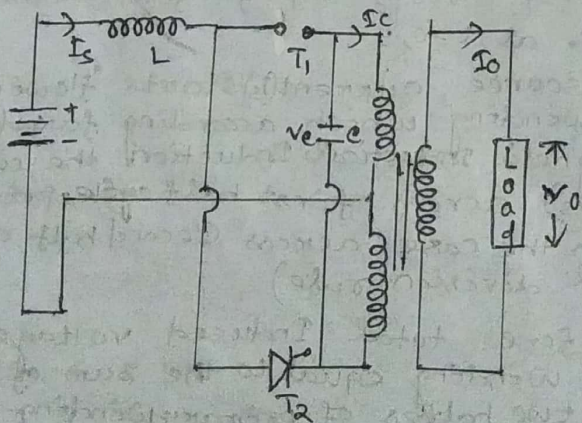

at  $t=t_1$

$T_2$  is ON as it is gated in

$T_1$  is OFF.

$$I_{T2} = I_s = I_o$$


$$I_{T1} = 0$$

$$\dot{e}_c = 0$$

$$V_c = -2V_s$$



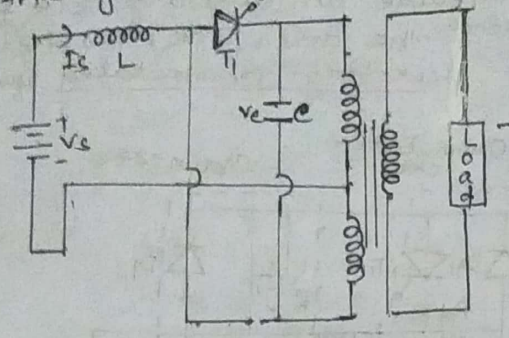Mode-04 at  $t=t_2$ , At this instant capacitor charging voltage  $V_c = -2V_s$  appear across  $T_2$  & Reverse biased it there by turning it off  
 ↳ Also this charging voltage appears across  $T_1$  & starts forward biasing it & aids the the gate signal to turn 'ON' it.




$T_1$  is ON as gated it.

$T_2$  is OFF.

$I_{T1} = I_s = I_o$

$I_{T2} = 0$


$V_o = V_s$

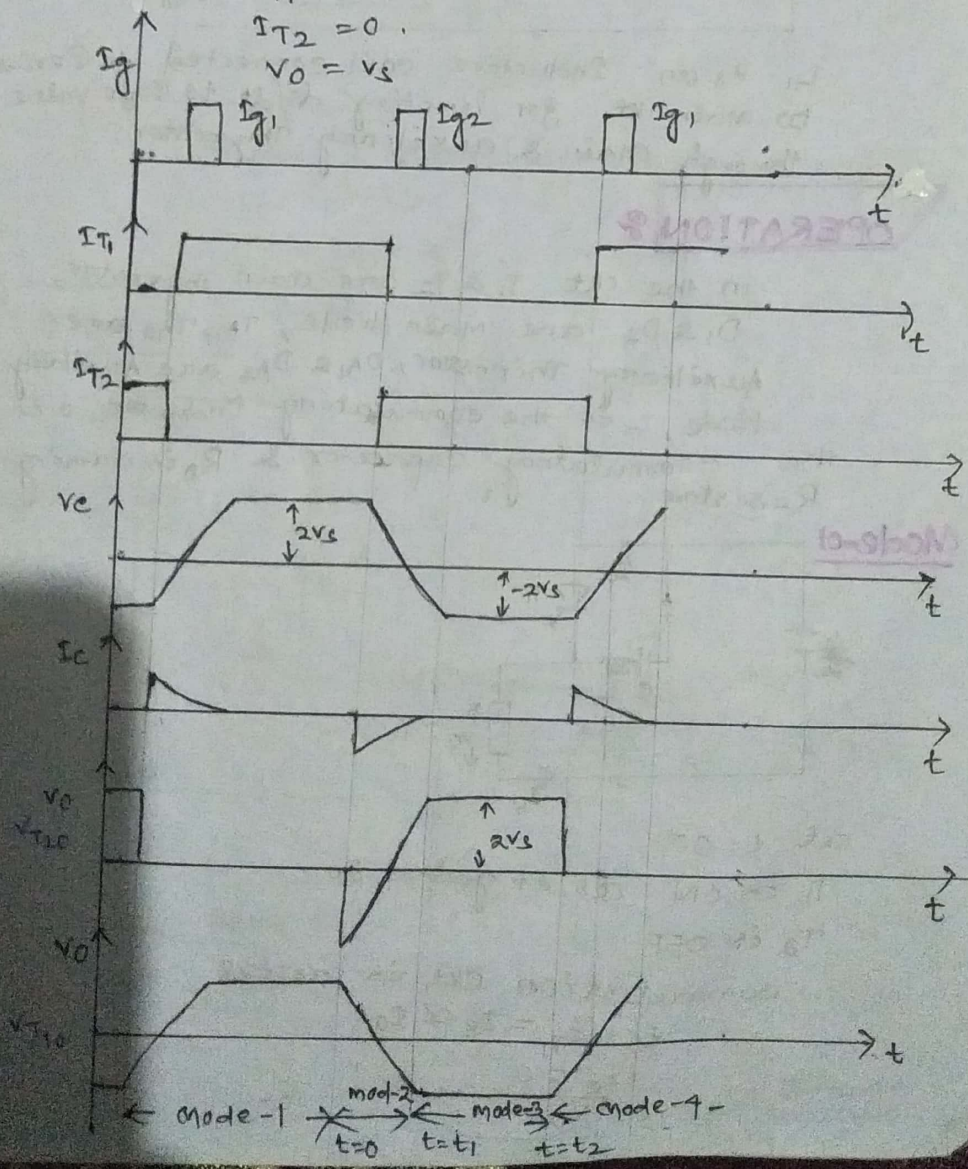


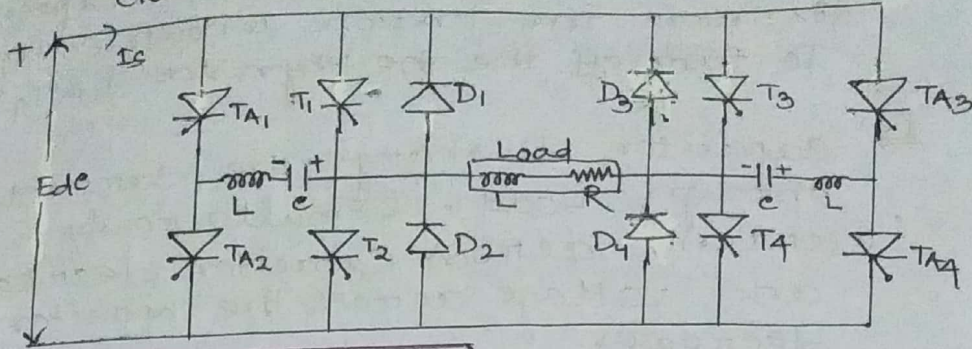
# VOLTAGE SOURCE FULL BRIDGE INVERTER

MC Mercey Impulse commutated 1- $\phi$  Bridge Ckt.




## CKT DESCRIPTION

It consists of four main Thyristors  $T_1, T_2, T_3$  &  $T_4$ . Diodes  $D_1, D_2, D_3$  &  $D_4$  commutation ckt consists of four auxiliary Thyristors  $TA_1, TA_2, TA_3$  &  $TA_4$ . Inductance & capacitance

Its operation may be explained in different four modes.
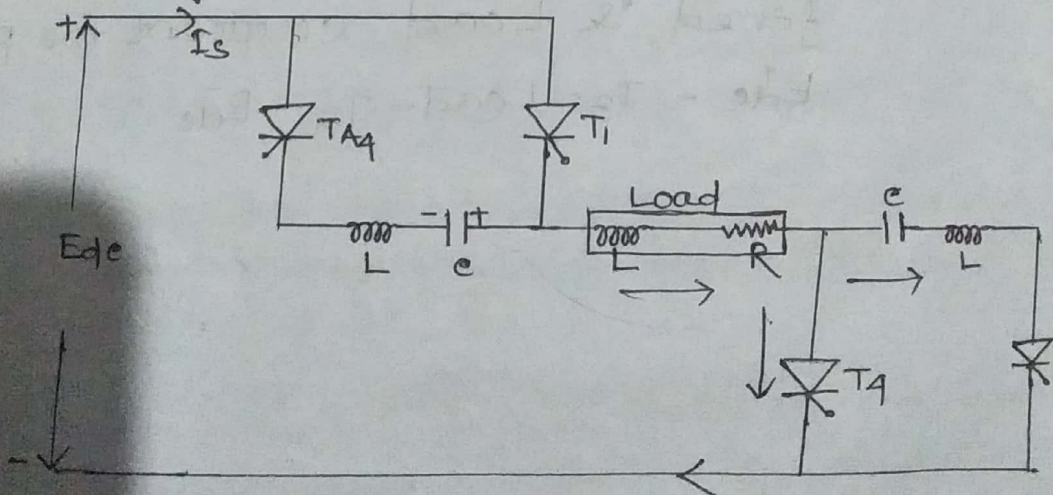
### MODE-01

Initially thyristors  $T_1, T_4, TA_1$  &  $TA_4$  are triggered & hence, they are made to conduct a load current  $I_o$ , whose direction is shown in fig. & capacitor is charged to a voltage  $V_c$



Load current follow the path  
 $E_{dc}^+ - T_1 - \text{Load} - T_4 - E_{dc}^-$



### MODE-02

For commutation process capacitor discharge the charge @ how in fig  
To turn off the thyristor  $T_1$  &  $T_4$

↳ Capacitor discharge the current through Load. Simultaneously current across capacitor decrease and voltage across the capacitor decreases.

### MODE-03

↳ When ever  $I_c < I_o$ , thyristor  $T_1$  &  $T_4$  Return to the forward blocking mode


↳ The Thyristor  $T_1$  &  $T_4$  return forward blocking mode.

↳ Again  $T_{A1}$  &  $T_{A4}$  followed the path.

### MODE-04

During this mode  $T_2$  &  $T_3$  are fired & Load current the path


$E_c - T_3 - \text{Load} - T_2 - E_c$

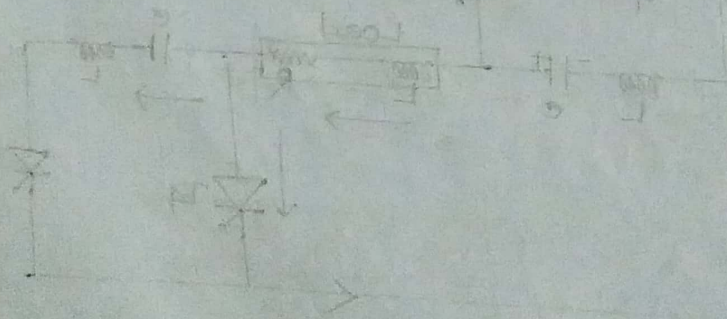


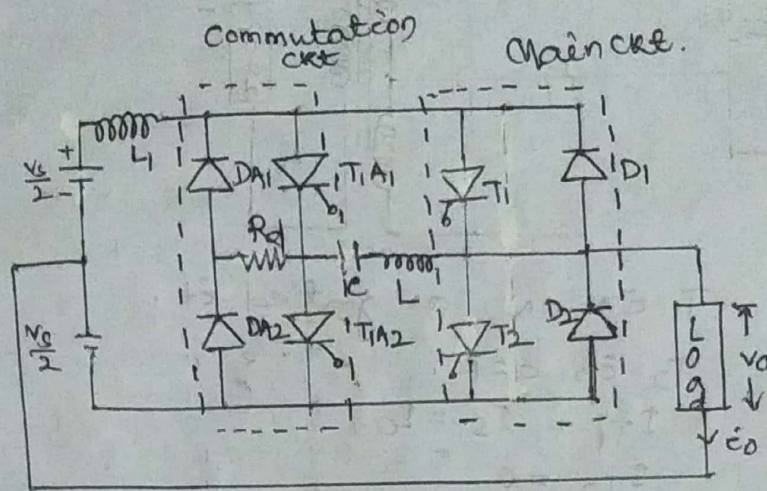
# M C MURRAY VOLTAGE SOURCE HALF BRIDGE INVERTER

- ↳ 1- $\phi$  Modified M.C. Murray Bridge Inverter basically a current commutated voltage source inverter.
- ↳ Its ckt include an auxiliary CCR for commutating the main CCR. So it is named as auxiliary commutated inverter.




$L_1$  is an Inductive coil connected in series to main ckt for limiting  $di/dt$  to safe value through main & auxiliary Thyristor.

## OPERATION

In the ckt  $T_1$  &  $T_2$  are main Thyristor,  $D_1$  &  $D_2$  are main diode,  $TA_1$ ,  $TA_2$  are Auxiliary Thyristor,  $DA_1$  &  $DA_2$  are Auxiliary diode,  $L_c$  is the commutating Inductor,  $C$  is the commutating capacitor, &  $R_d$  is damping Resistor.

### Mode-01

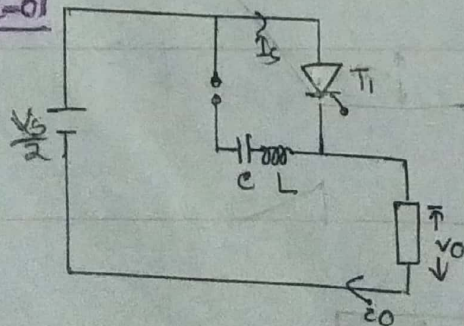

at  $t=0^-$

$T_1$  is ON as it gated on.

$T_2$  is OFF

commutation ckt is passive


$$\dot{e}_o = \dot{e}_{T_1} = I_s \approx I_o$$

$$\dot{e}_c = 0$$



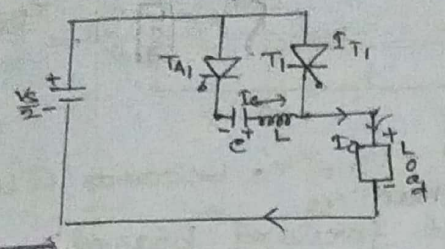**Mode-2**


at  $t=0$   
 $T_{A1}$  is ON  
 Capacitor starts charging  
 Since voltage drop across  $T_1$  Reverse biased  $D_1$



Here  
 $I_o = I_{T1} + I_{TA}$   
 $I_c = I_o$   
 $\Rightarrow I_c = I_{T1} + I_{TA}$

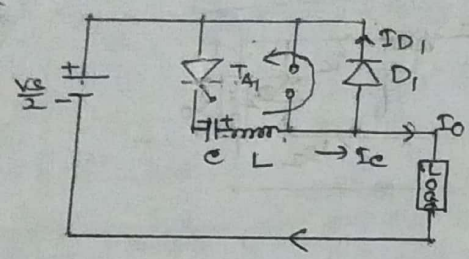**Mode-3**


AT  $t=t_1$   
 $T_1$  is turned off & diode ( $D_1$ ) is ON



Capacitor starts discharging through  $D_1$   
 $I_o = I_c - I_{D1}$   
 $I_c = I_{D1} + I_o$

*F.O. - 500M*

**Mode-4**

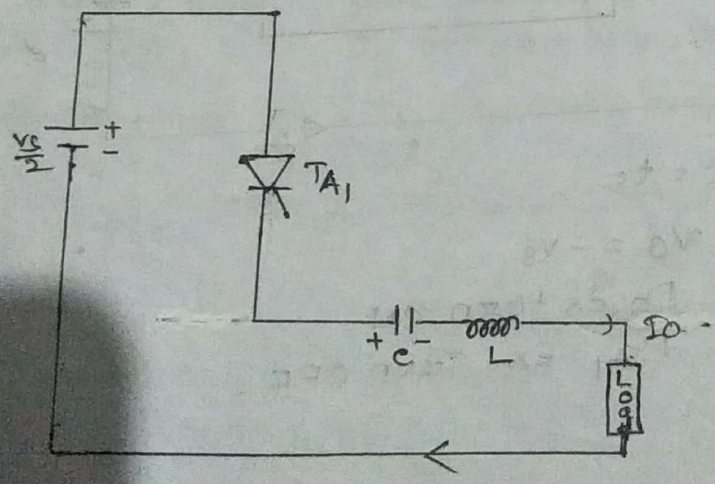


at  $t=t_2$   
 $D_1$  turned off  
 Here  $I_{T_{A1}} = I_c = I_o$

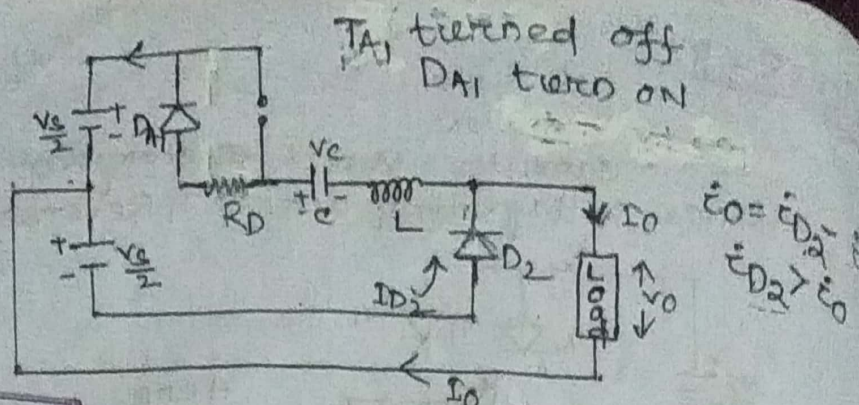**Mode-05**


AT  $t=t_3$   
 Here  $V_c = V_m$  (The energy stored in inductor is transferred to capacitor consequence capacitor is charged to peak voltage  $V_m$  at  $t_3$ )






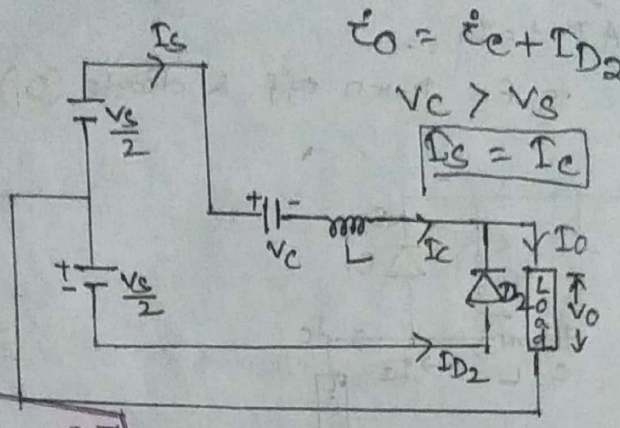**Mode-05**

AT  $t = t_3$ ,  $v_c$  becomes slightly more than  $v_s$   
 $D_2$  get forward biased



**Mode-06**

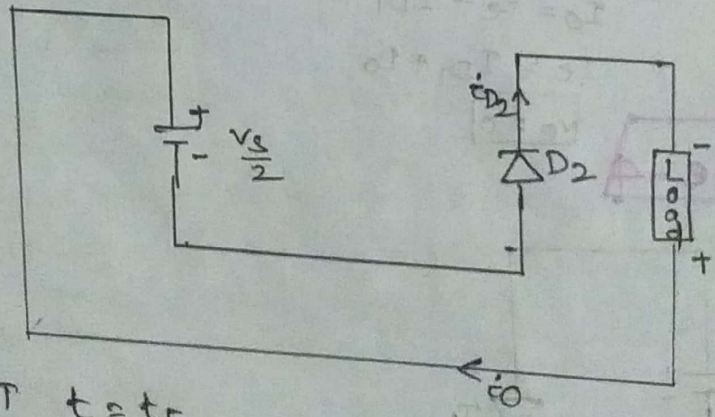


AT  $t = t_5$   
 $v_o = -v_s$   
 $D_2$  is turned ON  
 $D_1$  is turned OFF.




$i = i_{D2} - i_{D1}$   
 $D2 > E0$

ightly

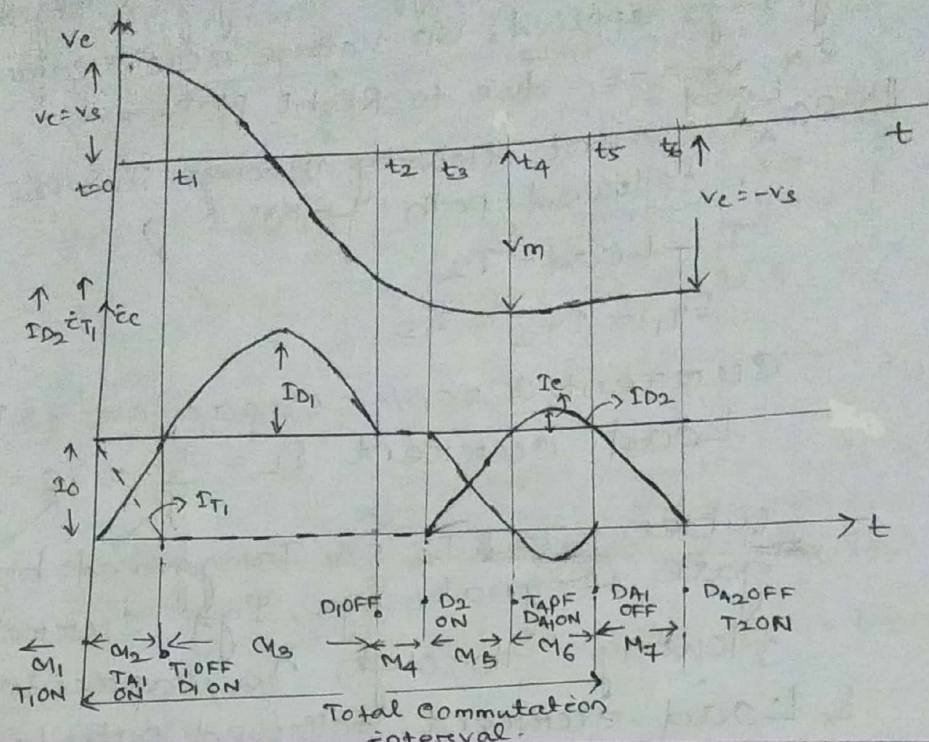

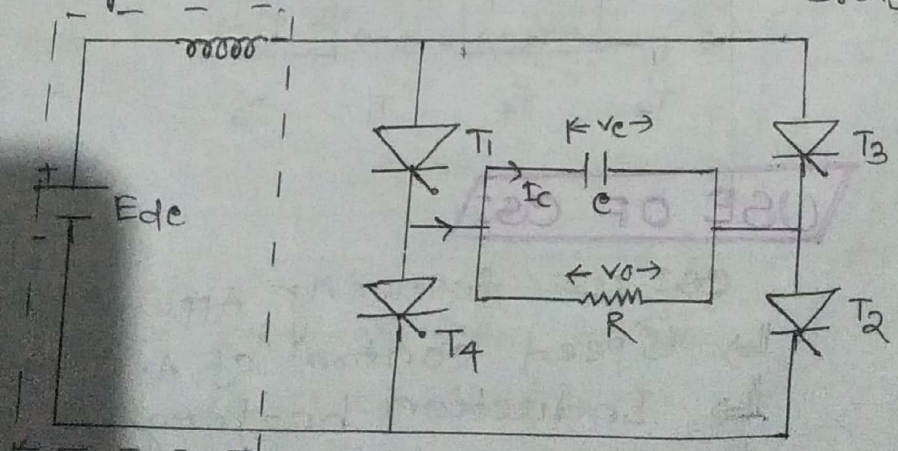**SINGLE PHASE CAPACITOR COMMUTATED CURRENT SOURCE INVERTER WITH R-LOAD**

- ↳ Single phase, current source bridge inverter with R-load. Capacitor 'C' in parallel with load is used for storing the charge for forced commutation of SCR.
- ↳ Thyristors  $T_1, T_2, T_3$  &  $T_4$  from the power Bridge.



↳ Constant Current Source 'L' is Large



↳ When  $T_1$  &  $T_2$  is triggered by gate signal  $I_{g1}, I_{g2}$  applied, so voltage across capacitor is  $V_c = -E_1$  due to right plate +ve.

↳ So <sup>Load</sup> current flowing through  $T_1$  &  $T_2$  is followed path like

$$T_1 - \text{Load} - T_2$$


$$I_{T1} = I_{T2} = I_s$$

Current across capacitor is  $I_c$   
Load current  $I_L = \frac{E_L}{R} = \frac{V_0}{R} = -\frac{V_c}{R}$

When  $T_3$  &  $T_4$  is triggered by gate signal  $I_{g3}, I_{g4}$  current flowing through  $T_3$ , capacitor & Load current followed path like

$T_3 = \text{Load} - T_4$ , Hence  $V_c = E_1$   
&  $I_{T3} = I_{T4} = I_s$

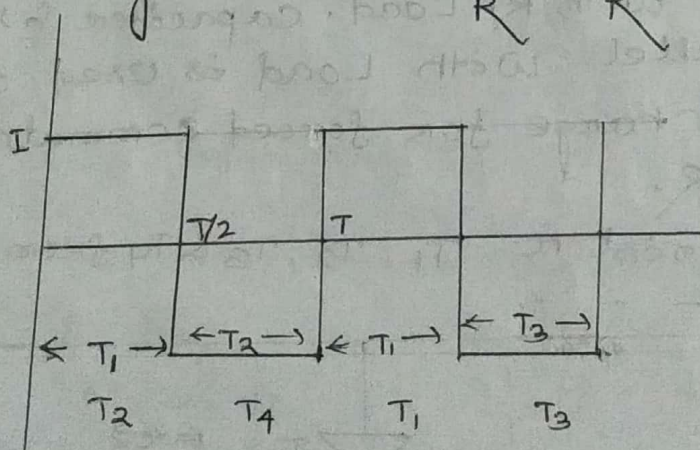again  $I_L = \frac{E_L}{R} = \frac{V_0}{R} = \frac{V_c}{R}$



### USE OF CSI

CSI use following Application.

- ↳ Speed control of A.C motor.
- ↳ Induction heating
- ↳ Synchronous motor starting
- ↳ Lagging VAR compensation.